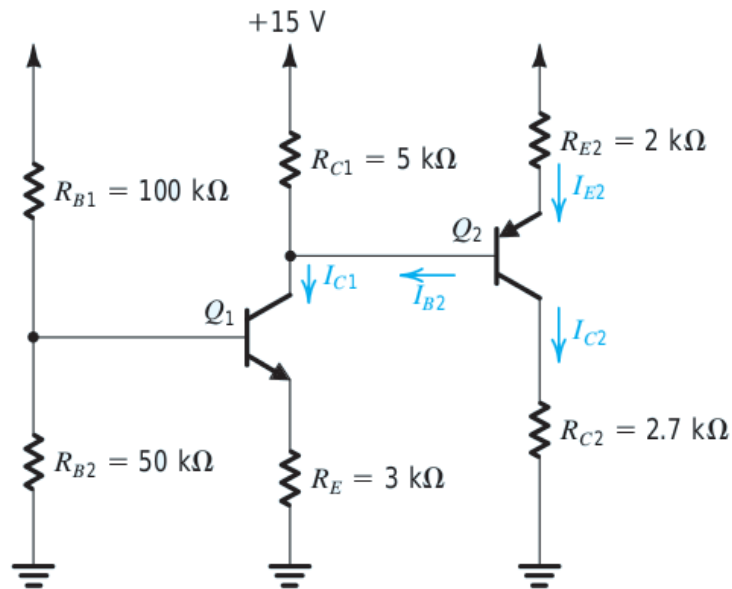


BJT Circuits at DC

Example 6.11


- We want to analyze the circuit in Fig. 6.29(a) to determine the voltages at all nodes and the currents through all branches. Assume $\beta = 100$ for both transistors.




BJT Circuits at DC

①/5

Example 6.11

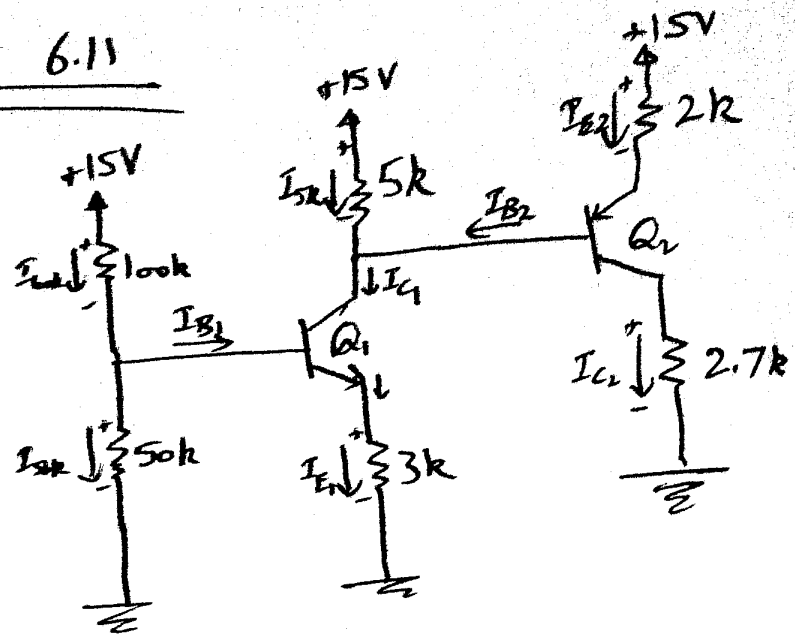

Q_1 is npn, Q_2 is pnp

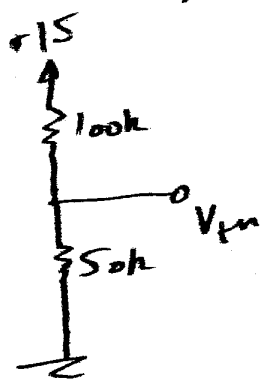

Finding
Thevenin Equivalent

$$\Rightarrow R_{th} = 100k // 50k$$


$$= 33.33k$$

by voltage divider

$$V_{th} = \frac{50k}{50k + 100k} \cdot 15V$$

$$= 5V$$

(245)

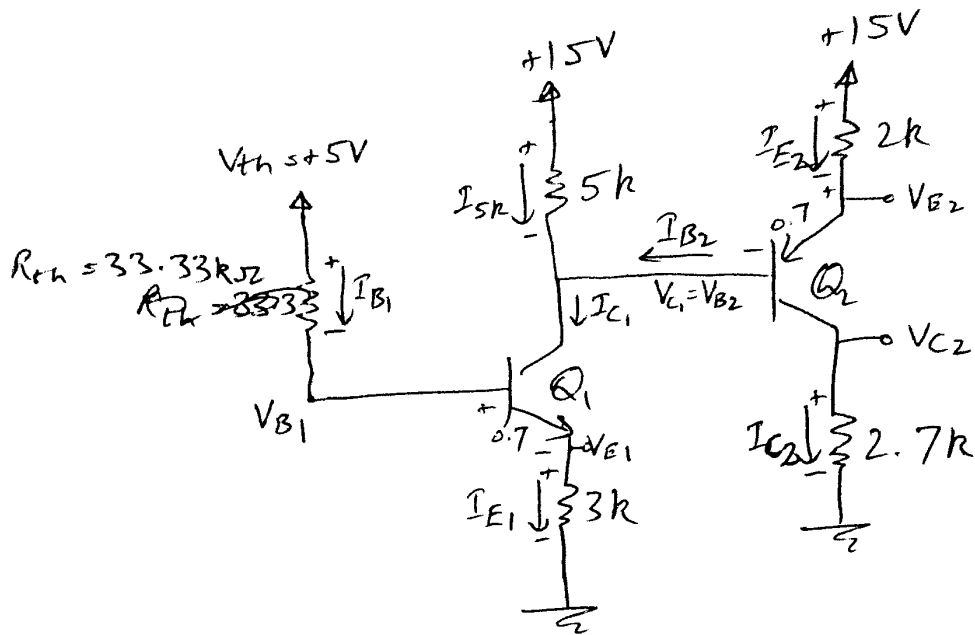

Assuming both Q_1 , Q_2 are in active mode

$$\text{here } \beta = \beta_1 = \beta_2 = 100, \quad \alpha = \alpha_1 = \alpha_2 = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.9901$$

KVL for Q_1

$$\Rightarrow 5 = (33.33k) I_{B1} + 0.7 + (3k) I_{E1}$$

$$\therefore I_{E1} = I_{C1} + I_{B1} = \beta I_{B1} + I_{B1} = (\beta + 1) I_{B1}$$

$$5 = (33.33k) I_{B1} + 0.7 + (3k)(\beta + 1) I_{B1}$$

$$5 - 0.7 = \{33.33k + 3k(\beta + 1)\} I_{B1}$$

$$4.3 = (33.33k + 3k(101)) I_{B1}$$

$$I_{B1} = \frac{4.3}{336.33k} = 0.0128 \text{ mA}$$

$$I_{E1} = (\beta + 1) I_{B1} = (101)(0.0128 \text{ mA}) = 1.293 \text{ mA}$$

$$I_{C1} = \beta I_{B1} = (100)(0.0128 \text{ mA}) = 1.28 \text{ mA}$$

(3/45)

By ohm's law

$$V_{E1} = (3k) I_{E1} = (3k)(1.293m) = 3.879V$$

By KVL

$$V_{B1} = 0.7 + V_{E1} = 0.7 + 3.879 = 4.579V$$

$$KCL \Rightarrow I_{5k} + I_{B2} = I_{C1}$$

$$I_{5k} = I_{C1} - I_{B2} = 1.28m - I_{B2} \rightarrow (1)$$

by ohm's law

$$15 - V_{C1} = (5k) I_{5k} \rightarrow (2)$$

$$15 - (5k) I_{5k} = V_{C1}$$

$$\text{also } V_{C1} = V_{B2}$$

Now for Q_2

Assume Active mode

KVL for Q_2

$$\Rightarrow 15 = (2k) I_{E2} + 0.7 + V_{B2}$$

$$15 - 0.7 = (2k) I_{E2} + V_{B2} \quad \because V_{B2} = V_{C1}$$

$$14.3 = (2k) I_{E2} + [15 - (5k) I_{5k}] \quad \because V_{C1} = 15 - (5k) I_{5k} \text{ because of (2)}$$

$$14.3 = (2k) I_{E2} + 15 - (5k)(1.28m - I_{B2})$$

 $\because \text{ of (1)}$

$$\text{as } I_{E2} = (\beta + 1) I_{B2} = 101 I_{B2}$$

$$\Rightarrow 14.3 = (2k)(101) I_{B2} + 15 - (5k)(1.28m) + (5k) I_{B2}$$

$$14.3 - 15 = (202k) I_{B2} - 6.4 + (5k) I_{B2}$$

$$14.3 - 15 + 6.4 = (202k + 5k) I_{B2}$$

(4/5)

$$5.7 = (207k) I_{B2}$$

$$I_{B2} = \frac{5.7}{207k} = 0.02754 \text{ mA}$$


$$I_{E2} = (\beta + 1) I_{B2} = (101)(0.02754 \text{ mA}) = 2.7815 \text{ mA}$$

$$I_{C2} = \beta I_{B2} = (100)(0.02754 \text{ mA}) = 2.754 \text{ mA}$$

$$\begin{aligned} \text{Eq. ①} \Rightarrow I_{S1} &= 1.28 \text{ mA} - I_{B2} \\ &= 1.28 \text{ mA} - 0.02754 \text{ mA} \\ &= 1.2525 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{Eq. ②} \Rightarrow V_{C1} &= 15 - (5k)(1.2525 \text{ mA}) \\ &= 8.7375 \text{ V} \end{aligned}$$

Thus for Q_1

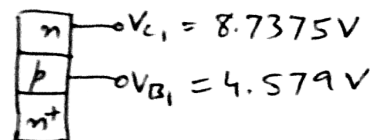

$$V_{C1} > V_{B1}$$

$\Rightarrow$ CBT of Q_1 is reverse biased
 $\Rightarrow Q_1$ is indeed in active mode.


for Q_2

by ohm's law

$$\begin{aligned} V_{C2} &= (I_{C2})(2.7k) = (2.754 \text{ mA})(2.7k) \\ &= 7.4358 \text{ V} \end{aligned}$$

$$V_{B2} = V_{C1} = 8.7375 \text{ V}$$

Thus for Q_2

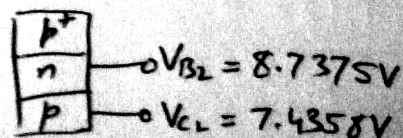

$$\text{Here } V_{B2} > V_{C2}$$

$\Rightarrow$ CBT of Q_2 is reverse biased $\Rightarrow Q_2$ is indeed in active mode.

BJT Circuits at DC

- by KVL

$$- V_{E2} = V_{B2} + 0.7 = 8.7375 + 0.7 = 9.4375V$$

- by ohm's law

$$- I_{50k} = \frac{V_{B1} - 0}{50k} = \frac{4.579}{50k} = 0.0916mA$$

- by ohm's law

$$- I_{100k} = \frac{15 - V_{B1}}{100k} = \frac{15 - 4.579}{100k} = 0.10421mA$$