

Lecture 5b


EE-215 Electronic Devices and Circuits

Asst Prof Muhammad Anis Ch

MOSFET Circuits at DC

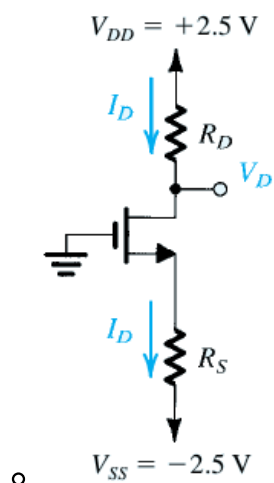
Example 5.3

- Design the circuit of Fig. 5.21, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $L = 1 \mu\text{m}$, and $W = 32 \mu\text{m}$. Neglect the channel-length modulation effect (i.e., assume that $\lambda = 0$).




Solution: Example 5.3


- here
 - $R_D = ?$, $R_S = ?$
 - $I_D = 0.4 \text{ mA}$, $V_D = 0.5 \text{ V}$,
 - $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $L = 1 \mu\text{m}$, $W = 32 \mu\text{m}$, $\lambda = 0$
 - As $V_D = 0.5 \text{ V}$, $I_D = 0.4 \text{ mA}$
 - Ohm's law $\Rightarrow R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4 \text{ mA}} = 5 \text{ k}\Omega$
 - As $I_D \neq 0 \Rightarrow$ the MOSFET is on
 - so the MOSFET can be in triode region or in saturation region

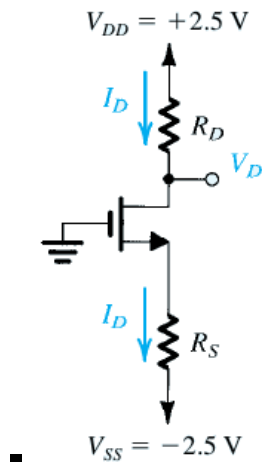

- so the MOSFET can be in triode region or in saturation region
 - As for triode region $v_{DS} < v_{OV} = v_{GS} - V_t$
 - and for saturation region $v_{DS} \geq v_{OV} = v_{GS} - V_t$
 - or $v_D \geq (v_G - V_t)$
 - here $v_D = 0.5$, $v_G = 0$, $V_t = 0.7 \Rightarrow v_G - V_t = 0 - 0.7$
 - $\Rightarrow 0.5 \geq -0.7$ thus the MOSFET is in saturation region
 - $i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) v_{OV}^2 = \frac{1}{2} 100 \mu \left(\frac{32}{1} \right) v_{OV}^2$
 - $i_D = 0.4m = \frac{1}{2} 100 \mu \left(\frac{32}{1} \right) v_{OV}^2$
 - $v_{OV}^2 = \frac{0.4m}{\frac{1}{2} 100 \mu \left(\frac{32}{1} \right)} = 0.25$

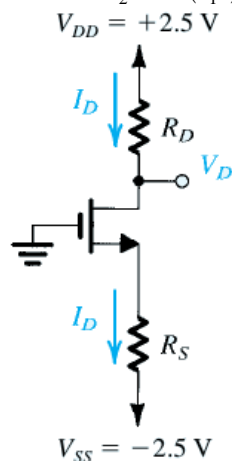


- $v_{OV} = \sqrt{0.25} = 0.5V$
 - $v_{OV} = v_{GS} - V_t = 0.5V \Rightarrow v_{GS} = V_t + 0.5 = 0.7 + 0.5 = 1.2V$
 - $v_G - v_S = 1.2V$
 - $0 - v_S = 1.2V$
 - $v_S = -1.2V$
 - by ohms' law
 - $R_S = \frac{v_S - V_{SS}}{I_D} = \frac{-1.2 - (-2.5)}{0.4m} = \frac{-1.2 + 2.5}{0.4m} = 3.25k\Omega$

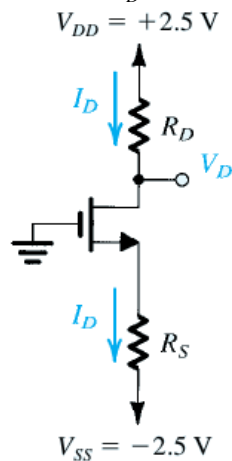

Example 5.4

- Figure 5.22 shows an NMOS transistor with its drain and gate terminals connected together. Find the $i - v$ relationship of the resulting two-terminal device in terms of the MOSFET parameters $k_n = k_n'(W/L)$ and V_{tn} . Neglect channel-length modulation (i.e., $\lambda = 0$). Note that this two-terminal device is known as a diode-


connected transistor.

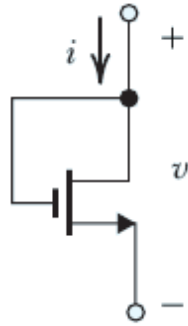

o **Figure 5.22**

Solution: Example 5.4


- here $v_G = v_D$
 - o as for saturation region
 - $v_{DS} \geq v_{GS} - V_t$
 - $v_D \geq v_G - V_t$
 - $v_D - v_G \geq -V_t$
 - $0 \geq -V_t$ which is true for an n-channel MOSFET (as V_t is +ve value)
 - $\Rightarrow$ the MOSFET is in saturation
 - i.e. $i_D = \frac{1}{2}k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$
 - from figure for $i = i_D$ and for $v = v_{GS}$
 - $i = \frac{1}{2}k_n' \left(\frac{W}{L} \right) (v - V_{tn})^2 = \frac{1}{2}k_n (v - V_{tn})^2$

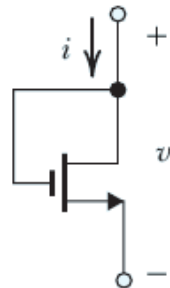

■ **Figure 5.22**

Exercise D5.9

- For the circuit in Fig. E5.9, find the value of R that results in $V_D = 0.8V$. The MOSFET has $V_{tn} = 0.5V$, $\mu_n C_{ox} = 0.4mA/V^2$, $\frac{W}{L} = \frac{0.72\mu m}{0.18\mu m}$ and $\lambda = 0$

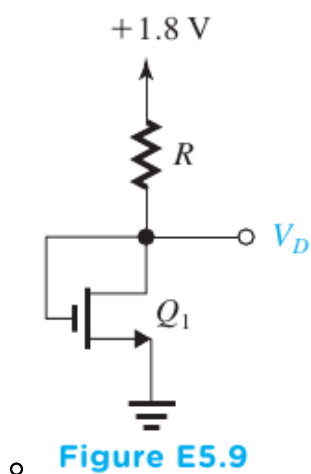**Solution: Exercise D5.9**

- here

- $V_D = 0.8V$

- $V_{in} = 0.5V$, $\mu_n C_{ox} = 0.4mA/V^2$, $\frac{W}{L} = \frac{0.72\mu m}{0.18\mu m}$ and $\lambda = 0$

- from the figure $v_G = v_D$

- $v_{DS} \geq v_{GS} - V_t$ for saturation region


- $v_D \geq v_G - V_t$

- $v_D - v_G \geq -V_t$

- $v_G - v_D \leq V_t$

- $0 \leq V_t$ which is true

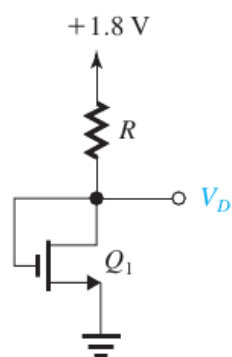- $\Rightarrow$ the MOSFET is in saturation



- Figure E5.9


- As $v_S = 0$

- $\Rightarrow v_{GS} = v_G - v_S = 0.8 - 0 = 0.8V \because v_G = v_D = 0.8V$

- $i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (v_{GS} - V_t)^2$

- $i_D = \frac{1}{2} 0.4m \left(\frac{0.72}{0.18} \right) (0.8 - 0.5)^2 = 72\mu A$

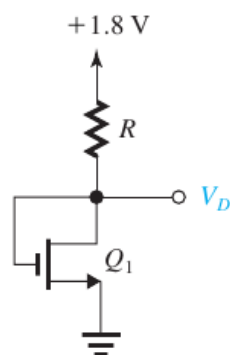
- $R = \frac{1.8 - V_D}{I_D} = \frac{1.8 - 0.8}{72\mu} = \frac{1}{72\mu} = 13.889k\Omega$



■ Figure E5.9

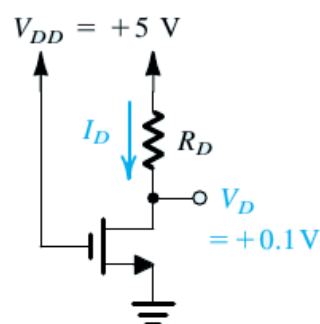Example 5.5


- Design the circuit in Fig. 5.23 to establish a drain voltage of 0.1 V . What is the effective resistance between drain and source at this operating point? Let $V_{tn} = 1\text{ V}$ and $k_n'(W/L) = 1\text{ mA/V}^2$.



○ Figure 5.23

Solution: Example 5.5

- here $v_{GS} = v_G - v_S = V_{DD} - 0 = 5 - 0 = 5\text{ V}$
 - $v_{DS} = v_D - v_S = 0.1 - 0 = 0.1\text{ V}$
 - $\Rightarrow v_{DS} < v_{GS} - V_t$
 - $0.1 < 5 - 1$
 - $0.1 < 4 \Rightarrow$ triode region
- for triode region
 - $i_D = k_n' \left(\frac{W}{L} \right) \left[(v_{GS} - V_{tn})v_{DS} - \frac{1}{2}v_{DS}^2 \right]$
 - $i_D = 1\text{ m} \left[(5 - 1)0.1 - \frac{1}{2}(0.1)^2 \right]$
 - $i_D = 1\text{ m} [0.4 - 0.005] = 0.395\text{ mA}$
 - $r_{DS} = \frac{v_{DS}}{i_D} = \frac{0.1}{0.395\text{ m}} = 253.16\Omega$
 - $R_D = \frac{V_{DD} - v_D}{i_D} = \frac{5 - 0.1}{0.395\text{ m}} = 12.405\text{ k}\Omega$

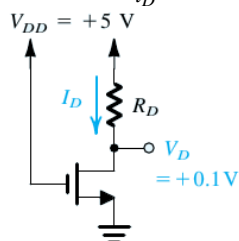

■ Figure 5.23

Exercise 5.11

- If in the circuit of Example 5.5 the value of R_D is doubled, find approximate values for I_D and V_D .

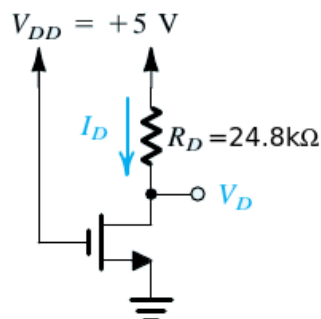


Figure for Exercise 5.11

Exercise 5.11: (Exact Analysis)

- Now R_D is doubled
 - $\Rightarrow R_D = 2 \times 12.4k\Omega = 24.8k\Omega$
 - As $V_{GS} > V_t$ i.e. $5 > 1 \Rightarrow$ mosfet is not cutoff
 - Assume Saturation mode
 - $I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} (1m)(4)^2 = \frac{16m}{2} = 8mA$
 - ohms law $\Rightarrow V_{DD} - V_D = I_D R_D$
 - $5 - V_D = (8m)(24.8k)$
 - $5 - V_D = 198.4$
 - $\Rightarrow 5 - 198.4 = V_D$
 - or $V_D = -193.4V$
 - Now for saturation $V_{DS} \geq V_{GS} - V_t \Rightarrow -193.4 \geq 5 - 1$ which is not true
 - $\Rightarrow$ MOSFET is not in saturation
 - Also note that $V_D = -193.4V$ is not possible in the given circuit as there is no -ve power supply present.
 - Assume triode mode
 - $\Rightarrow I_D = k_n' \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$
 - $I_D = 1m \left[(4) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$
 - by ohm's law $I_D = \frac{V_{DD} - V_{DS}}{R_D} = \frac{5 - V_{DS}}{24.8k}$
 - eliminating I_D from the above two equations
 - $\Rightarrow \frac{5 - V_{DS}}{24.8k} = 1m \left[4V_{DS} - \frac{1}{2} V_{DS}^2 \right]$
 - $5 - V_{DS} = 24.8 \left[4V_{DS} - \frac{1}{2} V_{DS}^2 \right]$
 - $5 - V_{DS} = 99.2V_{DS} - \frac{24.8}{2} V_{DS}^2$
 - $5 - V_{DS} = 99.2V_{DS} - 12.4V_{DS}^2$
 - $12.4V_{DS}^2 + 5 - V_{DS} - 99.2V_{DS} = 0$
 - $12.4V_{DS}^2 - 100.2V_{DS} + 5 = 0$
 - $V_{DS} = V_D \because V_S = 0$
 - $V_{DS} = V_D = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{100.2 \pm \sqrt{(-100.2)^2 - 4(12.4)(5)}}{2(12.4)}$
 - $\Rightarrow V_D = 4.0403 \pm 3.9901 = 8.0304V, 0.0502V$
 - $V_D = 8.0304V$ not possible $\because V_{DD} = +5V$ i.e. V_D can

not exceed 5V

$$\blacksquare \Rightarrow V_D = 0.0502V$$


$$\blacksquare I_D = \frac{5-V_{DS}}{24.8k} = \frac{5-V_D}{24.8k} = \frac{5-0.0502}{24.8k} = 0.19959mA$$

o now to verify the MOSFET is in triode region

$$\blacksquare V_{DS} < V_{GS} - V_t$$

$$\blacksquare \text{ or } 0.0502 < 4 \text{ which is TRUE}$$

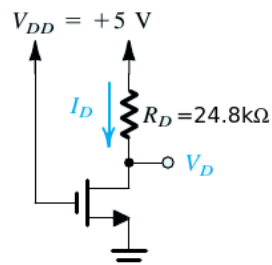$\blacksquare \Rightarrow$ MOSFET is indeed in triode region.



o Figure for Exercise 5.11

Exercise 5.11: (Approximate Analysis)

- Now R_D is doubled

$$o \Rightarrow R_D = 2 \times 12.4k\Omega = 24.8k\Omega$$

$$\blacksquare I_D = \frac{V_{DD}-V_D}{R} = \frac{5-V_D}{24.8k} \dots\dots(A)$$

$\blacksquare$ Approximation comes from assuming that r_{DS} stays the same as before

$$\blacksquare \text{ i.e. } r_{DS} = \frac{V_{DS}}{I_D} = 253\Omega$$


$$\blacksquare \Rightarrow I_D = \frac{V_{DS}}{r_{DS}} = \frac{V_D-V_S}{253} = \frac{V_D}{253} \dots\dots(B)$$

$\blacksquare$ (A) and (B)

$$\blacksquare \Rightarrow \frac{5-V_D}{24.8k} = \frac{V_D}{253} \Rightarrow \frac{5}{24.8k} - \frac{V_D}{24.8k} = \frac{V_D}{253}$$

$$\blacksquare \frac{5}{24.8k} - \frac{V_D}{24.8k} = \frac{V_D}{253} \Rightarrow \frac{5}{24.8k} = \frac{V_D}{253} + \frac{V_D}{24.8k}$$
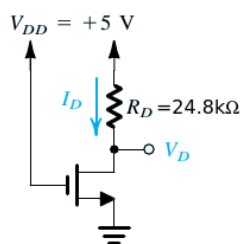
$$\blacksquare V_D = \left(\frac{5}{24.8k} \right) / \left(\frac{1}{253} + \frac{1}{24.8k} \right) = 0.0505V$$




$\blacksquare$ Figure for Exercise 5.11

$$o \text{ and from (A), } I_D = \frac{5-V_D}{24.8k} = \frac{5-0.0505}{24.8k} = 0.19958mA$$

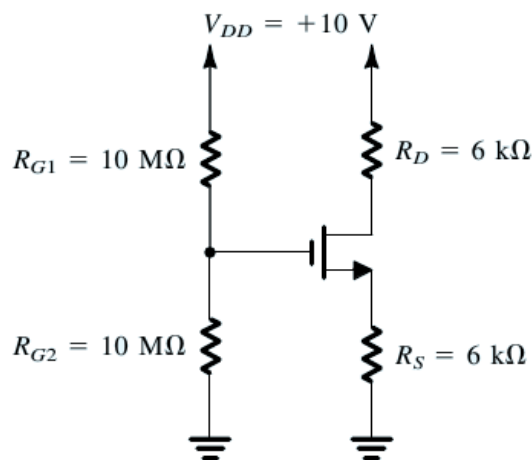Example 5.6

- Analyze the circuit shown in Fig. 5.24(a) to determine the voltages at all nodes and the currents through all branches. Let $V_{tn} = 1V$ and $k_n'(W/L) = 1mA/V^2$. Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$).



o

(a)

Solution: Example 5.6

- here

- o $V_{tn} = 1V$, $k_n'(W/L) = 1mA/V^2$, $\lambda = 0$

- as no current flows into the gate terminal
- by voltage divider


- $v_G = \frac{R_{G2}}{R_{G1} + R_{G2}} V_{DD} = \frac{10M}{20M} (10) = 5V$

- $I_{R_{G1}} = I_{R_{G2}} = \frac{v_G - 0}{R_{G2}} = \frac{5}{10M} = 0.5\mu A$

- As a +ve gate voltage exists, it is expected

- $= \Rightarrow$ the transistor is ON

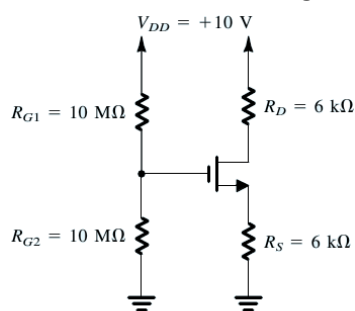
- however, we don't know whether it is operating in triode or saturation region



(a)

- let's solve by assuming the NMOS transistor is operating in saturation region,
- o and then check the validity of our assumption.

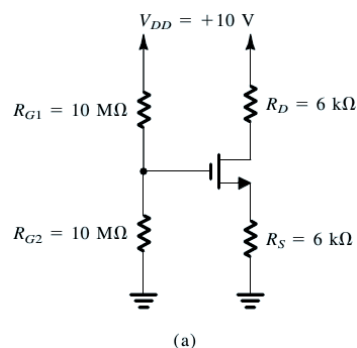- if our assumption turns out to be invalid,
 - we will have to solve the problem again for the triode region of operation.
- thus for saturation region,
 - $i_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$
 - $I_D = \frac{1}{2} (1m) (V_G - V_S - V_{tn})^2$
 - $I_D = 0.5m(5 - V_S - 1)^2$
 - $I_D = 0.5m(4 - V_S)^2$



$$\bullet I_D = 0.5m(4 - V_S)^2$$

$$\circ \text{ also } I_D = \frac{V_S - 0}{6k} = \frac{V_S}{6k} \Rightarrow V_S = (6k)I_D$$

■ substitute V_S into above expression for I_D

$$\blacksquare \Rightarrow I_D = 0.5m(4 - V_S)^2 = 0.5m(4 - (6k)I_D)^2$$

$$\blacksquare I_D = 0.5m(16 + (36M)I_D^2 - 2(4)(6k)I_D)$$

$$\blacksquare I_D = 0.5m(16 + (36M)I_D^2 - 2(4)(6k)I_D)$$

$$\blacksquare I_D = 8m + (18k)I_D^2 - 24I_D$$


$$\blacksquare 25I_D = 8m + (18k)I_D^2$$

$$\blacksquare (18k)I_D^2 - 25I_D + 8m = 0$$

■ this quadratic equation has the solution of

$$\blacksquare I_D = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{25 \pm \sqrt{(25)^2 - 4(18k)(8m)}}{2(18k)}$$
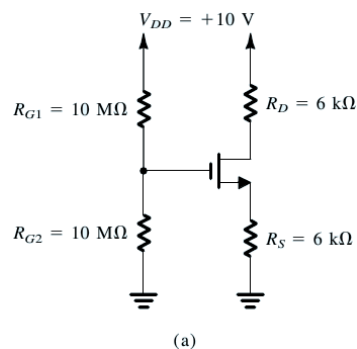
$$\blacksquare I_D = \frac{25 \pm 7}{36k} = 0.89mA, 0.5mA$$



$$\bullet I_D = \frac{25 \pm 7}{36k} = 0.89mA, 0.5mA$$

○ As $V_S = (6k)I_D$

$$\blacksquare \Rightarrow V_S = 5.34V \text{ for } I_D = 0.89mA$$

$$\blacksquare \text{ and } V_S = 3V \text{ for } I_D = 0.5mA$$

■ Note that for $V_S = 5.34V$ ($I_D = 0.89mA$)

$$\Rightarrow V_{GS} = 5 - 5.34 = -0.34$$


■ $\Rightarrow$ the MOSFET is off, so no I_D can't be equal to 0.89mA

■ thus this case is invalid


$$\blacksquare \Rightarrow V_S = 3V \text{ and } I_D = 0.5mA$$

$$\blacksquare V_{GS} = 5 - 3 = 2V$$
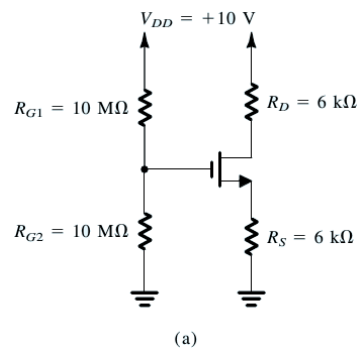
$$\blacksquare V_{GS} - V_{th} = 2 - 1 = 1V$$




- As $I_D = \frac{V_{DD} - V_D}{R_D} = \frac{10 - V_D}{6k}$
 - $\Rightarrow I_D = \frac{V_{DD} - V_D}{R_D} = \frac{10 - V_D}{6k}$
 - $0.5m = \frac{10 - V_D}{6k}$
 - $3 = 10 - V_D \Rightarrow V_D = 10 - 3 = 7V$
 - $V_{DS} = V_D - V_S = 7 - 3 = 4V$
 - $\Rightarrow$ here $V_{DS} = 4V$, $V_{GS} - V_t = 2 - 1 = 1V$
 - $\Rightarrow V_{DS} > V_{GS} - V_t$
 - i.e. $4V > 1V$
 - $\Rightarrow$ the initial assumption was correct, the transistor is in saturation region.

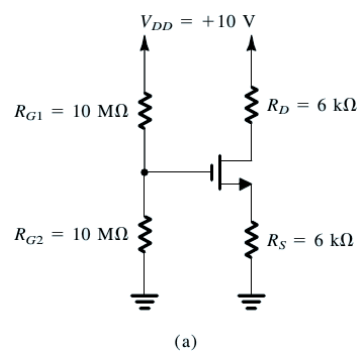

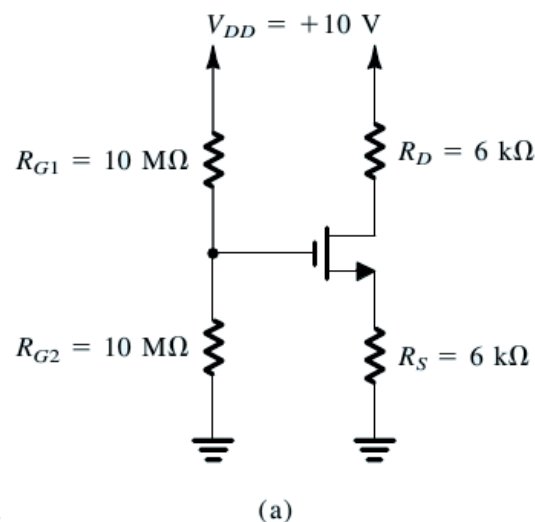Exercise 5.12

- For the circuit of Fig. 5.24, what is the largest value that R_D can have while the transistor remains in the saturation mode?



◦

Solution: Exercise 5.12

- for Saturation mode

- $v_{DS} \geq v_{GS} - V_t$

- or $v_D \geq v_G - V_t$

- for $\lambda = 0$, I_D remains constant in saturation region w.r.t v_{DS}


- as $R_D = \frac{V_{DD} - V_D}{I_D}$

- R_D is largest when V_D is smallest. As V_{DD} and I_D are constants.

- $\Rightarrow R_D = ?$ when $V_D = V_G - V_t = 5 - 1 = 4V$

- $R_D = \frac{V_{DD} - V_D}{I_D} = \frac{10 - 4}{I_D} = \frac{6}{I_D}$

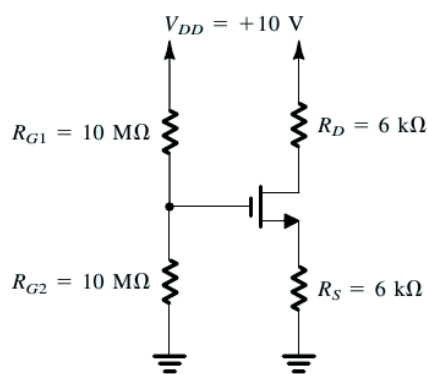- where $i_D = \frac{1}{2}k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$



(a)

- $i_D = \frac{1}{2}k_n' \left(\frac{W}{L} \right) (v_{GS} - V_{tn})^2$

- As R_S has not changed, $\Rightarrow v_{GS}$ is not changed


- $I_D = 0.5m(V_G - V_S - 1)^2 = 0.5m(5 - V_S - 1)^2 = 0.5m(4 - V_S)^2$

- also $I_D = \frac{V_S - 0}{6k} \Rightarrow V_S = I_D 6k$

- these two equations have already been solved in Example 5.6

- $\Rightarrow I_D = 0.5mA$

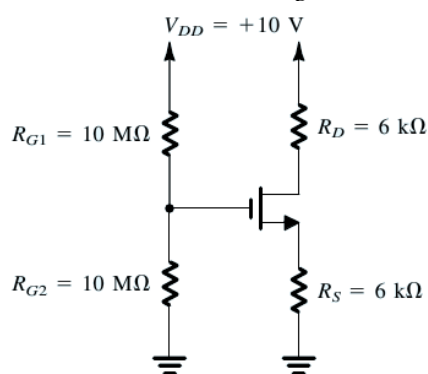- $\Rightarrow R_D = \frac{6}{I_D} = \frac{6}{0.5m} = 12k\Omega$



(a)

Example 5.7

- Design the circuit of Fig. 5.25 so that the transistor operates in saturation with

$I_D = 0.5\text{mA}$ and $V_D = +3\text{V}$. Let the enhancement-type PMOS transistor have $V_{tp} = -1\text{V}$ and $k_p'(W/L) = 1\text{mA/V}^2$. Assume $\lambda = 0$. What is the largest value that R_D can have while maintaining saturation-region operation?

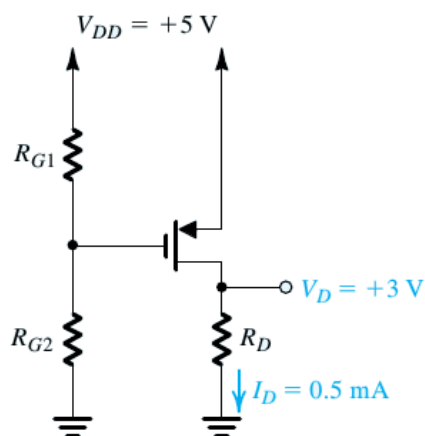


Figure 5.25 Circuit for Example 5.7.

Solution: Example 5.7

• here

◦ saturation region and $I_D = 0.5\text{mA}$

■ $V_{tp} = -1\text{V}$, $k_p'\left(\frac{W}{L}\right) = 1\text{mA/V}^2$, $\lambda = 0$

■ in saturation region

■ $i_D = \frac{1}{2}k_p'\left(\frac{W}{L}\right)(v_{SG} - |V_{tp}|)^2$

■ $0.5\text{mA} = \frac{1}{2}(1\text{mA})(v_{SG} - 1)^2$

■ $0.5\text{mA} = (0.5\text{mA})(v_{SG} - 1)^2$

■ $(v_{SG} - 1)^2 = 1 \Rightarrow v_{SG} - 1 = \pm 1$

■ or $v_{SG} = 1 \pm 1 = 2, 0$

■ $v_{SG} = 0$ doesnot make any sense as it means the device is cutoff but the given $I_D = 0.5\text{mA}$, so the device cannot be cutoff

■ $\Rightarrow V_{SG} = 2\text{V}$

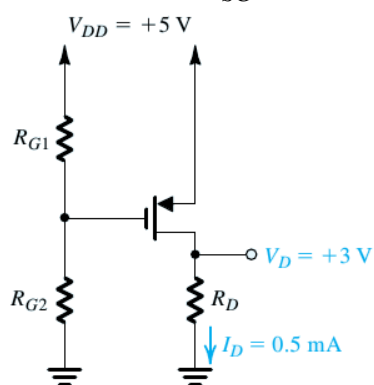


Figure 5.25 Circuit for Example 5.7.

• $V_{SG} = 2\text{V}$

◦ $V_S - V_G = 2\text{V}$

■ or $5 - V_G = 2\text{V}$

■ $V_G = 5 - 2 = 3\text{V}$

■ from the figure

$$\blacksquare V_G = \frac{R_{G2}}{R_{G1}+R_{G2}} V_{DD} \text{ and } \frac{5}{I_{R_{G1}}} = R_{G1} + R_{G2}$$

$$\blacksquare \text{ for } I_{R_{G1}} = 1\mu\text{A} \Rightarrow R_{G1} + R_{G2} = \frac{5}{1\mu} = 5\text{M}\Omega$$

$$\blacksquare V_G = \frac{R_{G2}}{R_{G1}+R_{G2}} V_{DD} \Rightarrow \frac{3}{5} = \frac{R_{G2}}{R_{G1}+R_{G2}} = \frac{R_{G2}}{5\text{M}} \Rightarrow R_{G2} = \frac{3}{5} \times 5\text{M} = 3\text{M}\Omega$$

$$\blacksquare R_{G1} = 5\text{M} - R_{G2} = 2\text{M}\Omega$$

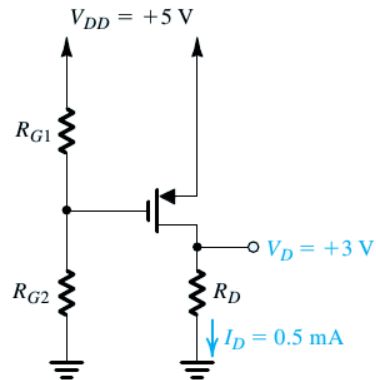


Figure 5.25 Circuit for Example 5.7.

• for saturation

$$\circ v_{SD} \geq v_{SG} - |V_{tp}|$$

$$\blacksquare v_S - v_D \geq v_S - v_G - |V_{tp}|$$

$$\blacksquare -v_D \geq -v_G - |V_{tp}|$$

$$\blacksquare -v_D \geq -v_G - 1$$

$$\blacksquare v_D \leq v_G + 1$$

■ at the edge (i.e. at the start of saturation region)

$$\blacksquare v_D = v_G + 1 = 3 + 1 = 4\text{V}$$

$$\blacksquare \Rightarrow R_D = \frac{v_D - 0}{I_D} = \frac{4 - 0}{0.5\text{mA}} = 8\text{k}\Omega$$

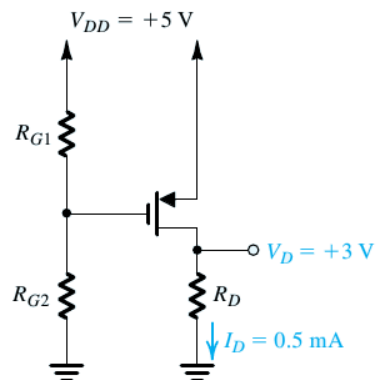


Figure 5.25 Circuit for Example 5.7.