


Lecture 7a

EE-215 Electronic Devices and Circuits


Asst Prof Muhammad Anis Ch

Small-Signal Equivalent Circuit Models

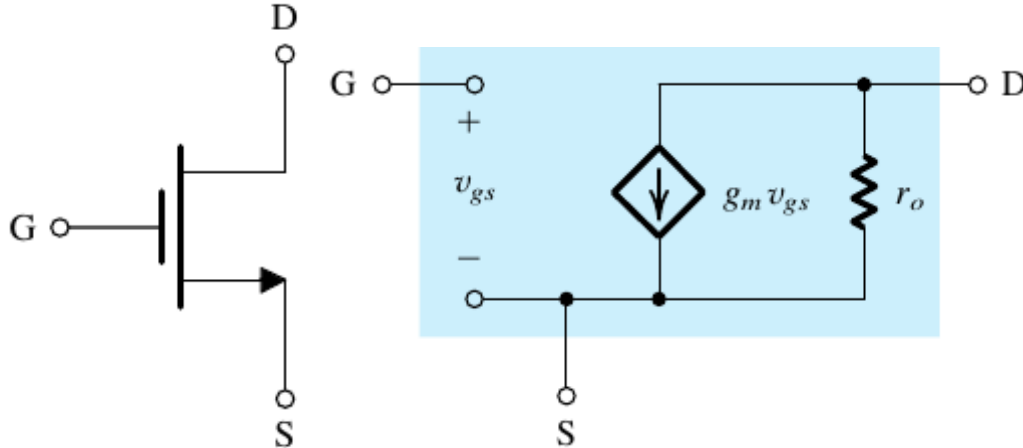- we had already seen the small-signal equivalent circuit model (hybrid- π model) for an NMOS transistor



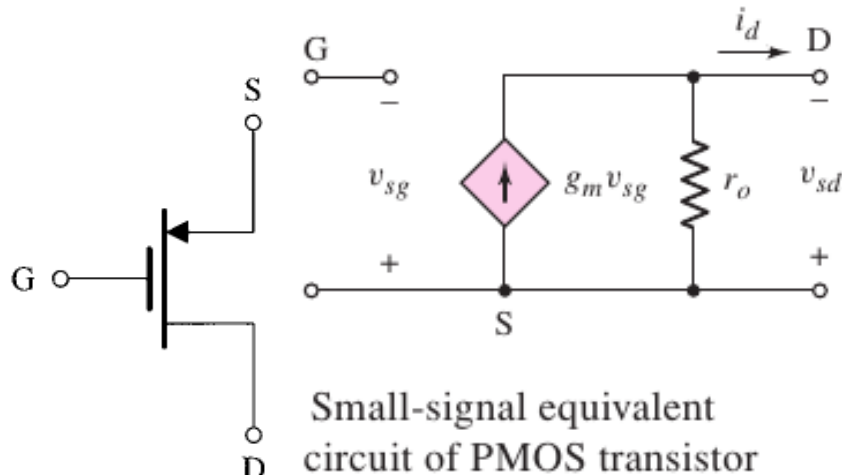
- also for PMOS transistor, the MOSFET acts as a voltage controlled current source.
 - thus the small-signal model for the p-channel MOSFET can be given as



- In the small-signal model of PMOS transistor,
 - if we substitute, $v_{sg} = -v_{gs}$

- $\Rightarrow g_m v_{sg} = -g_m v_{gs}$
- i.e. if the control voltage polarity is reversed, then the dependent current direction is also reversed.

○ also $v_{sd} = -v_{ds}$

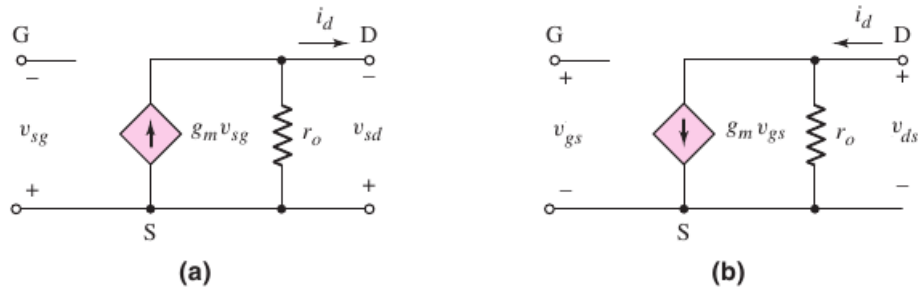


Small signal equivalent circuit of a p-channel MOSFET showing (a) the conventional voltage polarities and current directions and (b) the case when the voltage polarities and current directions are reversed.

- thus the resultant equivalent circuit (fig b) for the PMOS transistor is exactly the same as that of the NMOS transistor
 - we conclude that the small-signal equivalent circuit model (hybrid- π model) is
 - exactly the same for both the NMOS and the PMOS transistors

The T Equivalent-Circuit Model

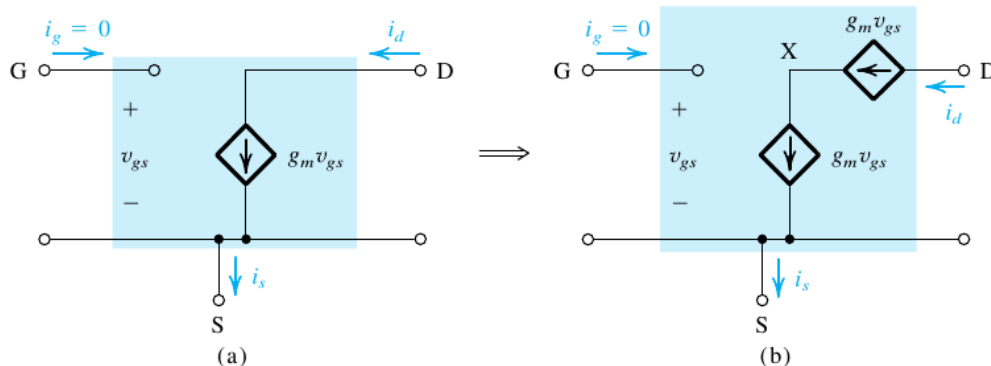
- A simple circuit transformation can lead to an alternative
 - equivalent circuit model for a MOSFET
 - we start with the hybrid- π model



- here we have placed a 2nd $g_m v_{gs}$ current source in series with the original controlled source.
- Note that, this new current source doesnot change the terminal currents and is thus allowed
- the new node X, can be connected to the gate.


◦ As because of KCL, still the gate current $i_g = 0$.

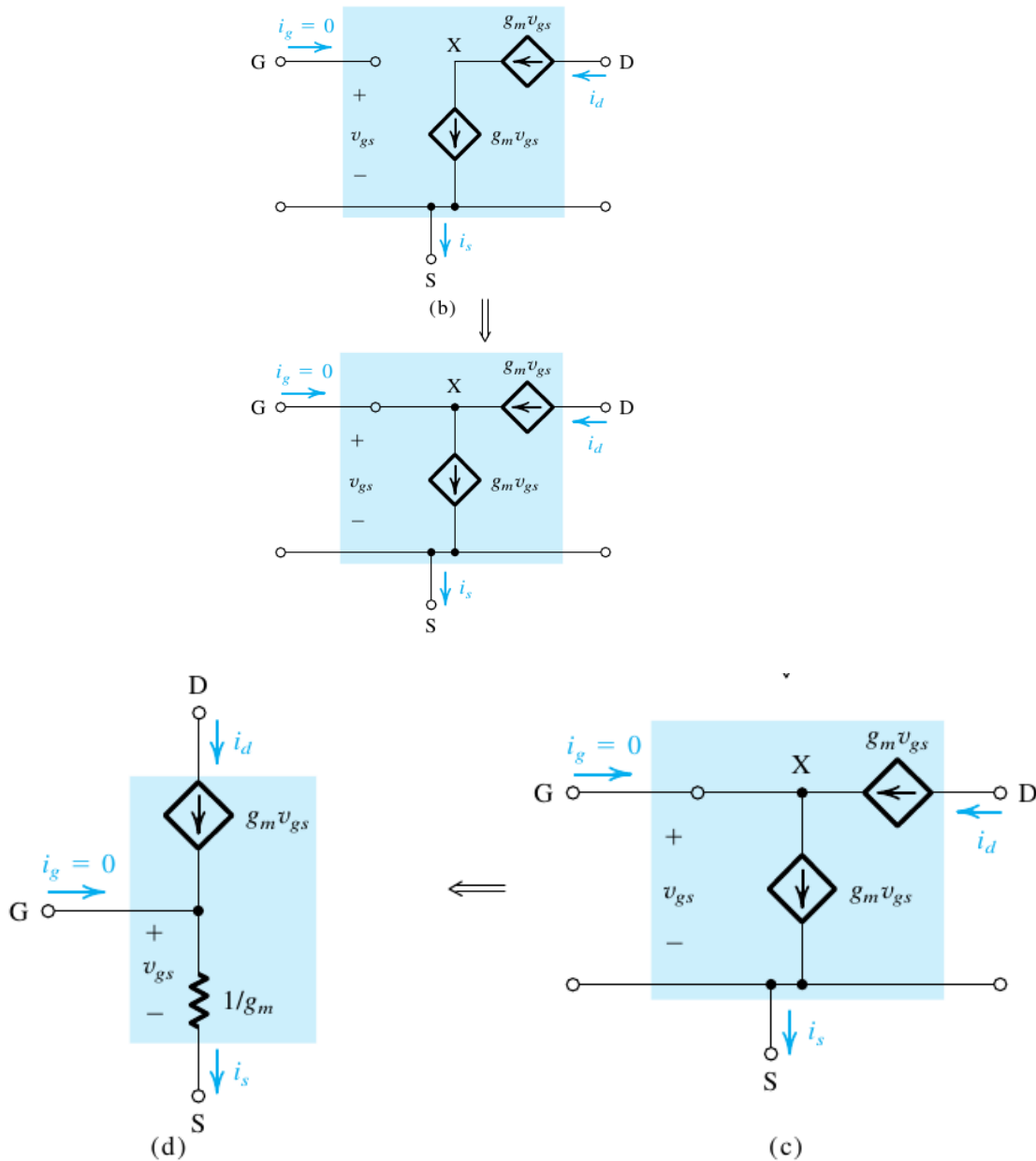■ so the gate current is still zero (i.e. this connection doesnot change the terminal characteristics)




- Note that, here we have a controlled current source $g_m v_{gs}$
 - whose current is controlled by the control voltage v_{gs}
 - where v_{gs} is across itself
 - $\Rightarrow$ this current source can be replaced by a resistor of value $\frac{v_{gs}}{g_m v_{gs}} = \frac{1}{g_m}$
- Note that the resistance between the gate and the source,

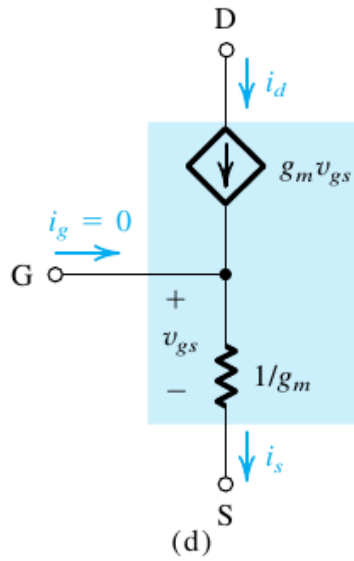- looking in to the source terminal is $1/g_m$
 - and looking in to the gate terminal is infinite



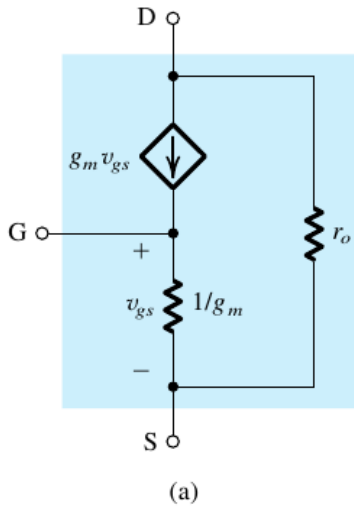- if the channel-length modulation effect cannot be ignored,
 - we can include r_o in the T-model between the drain and the source terminal



- Also we can have an alternative representation of the T model,
 - where we can replace the voltage-controlled current source by
 - a current controlled current source

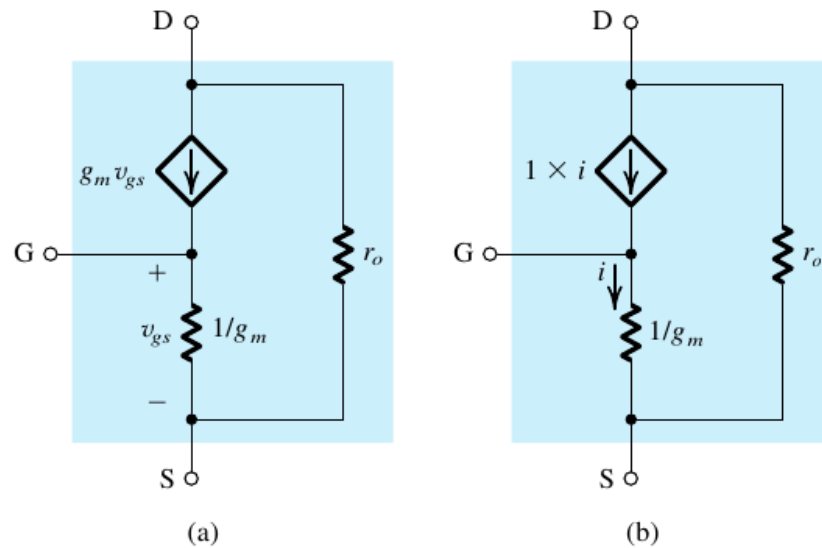


Figure 5.41 (a) The T model of the MOSFET augmented with the drain-to-source resistance r_o . (b) An alternative representation of the T model.

Small-Signal Operation and Models

Table 5.3 Small-Signal Equivalent-Circuit Models for the MOSFET

Small-Signal Parameters

NMOS transistors

Transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$$


Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$

PMOS transistors


Same formulas as for NMOS except using $|V_{OV}|$, $|V_A|$, and replacing μ_n with μ_p .

Small-Signal Equivalent Circuit Models

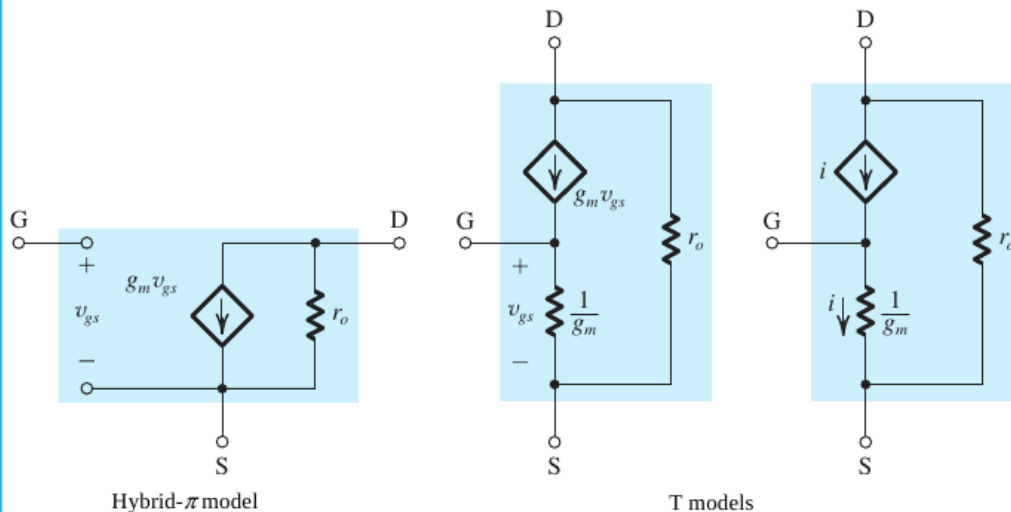

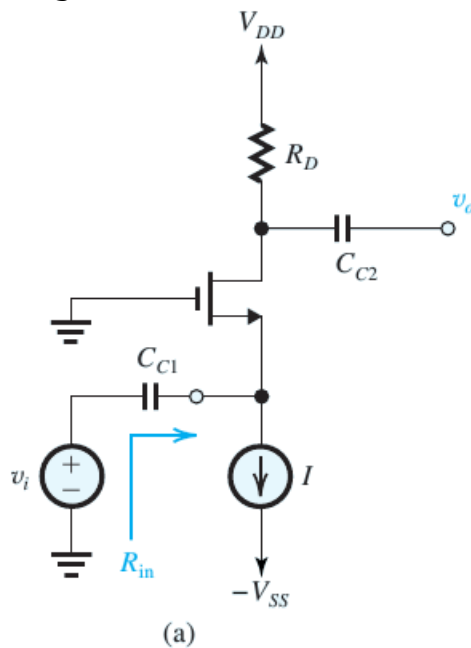Example 5.11

- Figure 5.42(a) shows a MOSFET amplifier biased by a constant-current source I . Assume that the values of I and R_D are such that the MOSFET operates in the saturation region. The input signal v_i is coupled to the source terminal by utilizing a large capacitor C_{C1} . Similarly, the output signal at the drain is taken through a large coupling capacitor C_{C2} . Find the input resistance R_{in} and the voltage gain v_o/v_i . Neglect channel-length modulation.



Solution:

- here $\lambda = 0$, $R_{in} = ?$, $A_v = \frac{v_o}{v_i} = ?$
 - as an ac source is connected at the source terminal of the MOSFET, it is more convenient to use T-model.
 - thus for ac analysis,
 - suppress dc sources i.e. V_{DD} is replaced by short circuit
 - and I is replaced by an open circuit
 - C_{C1} , C_{C2} are replaced by short circuits
 - MOSFET is replaced by its T-model


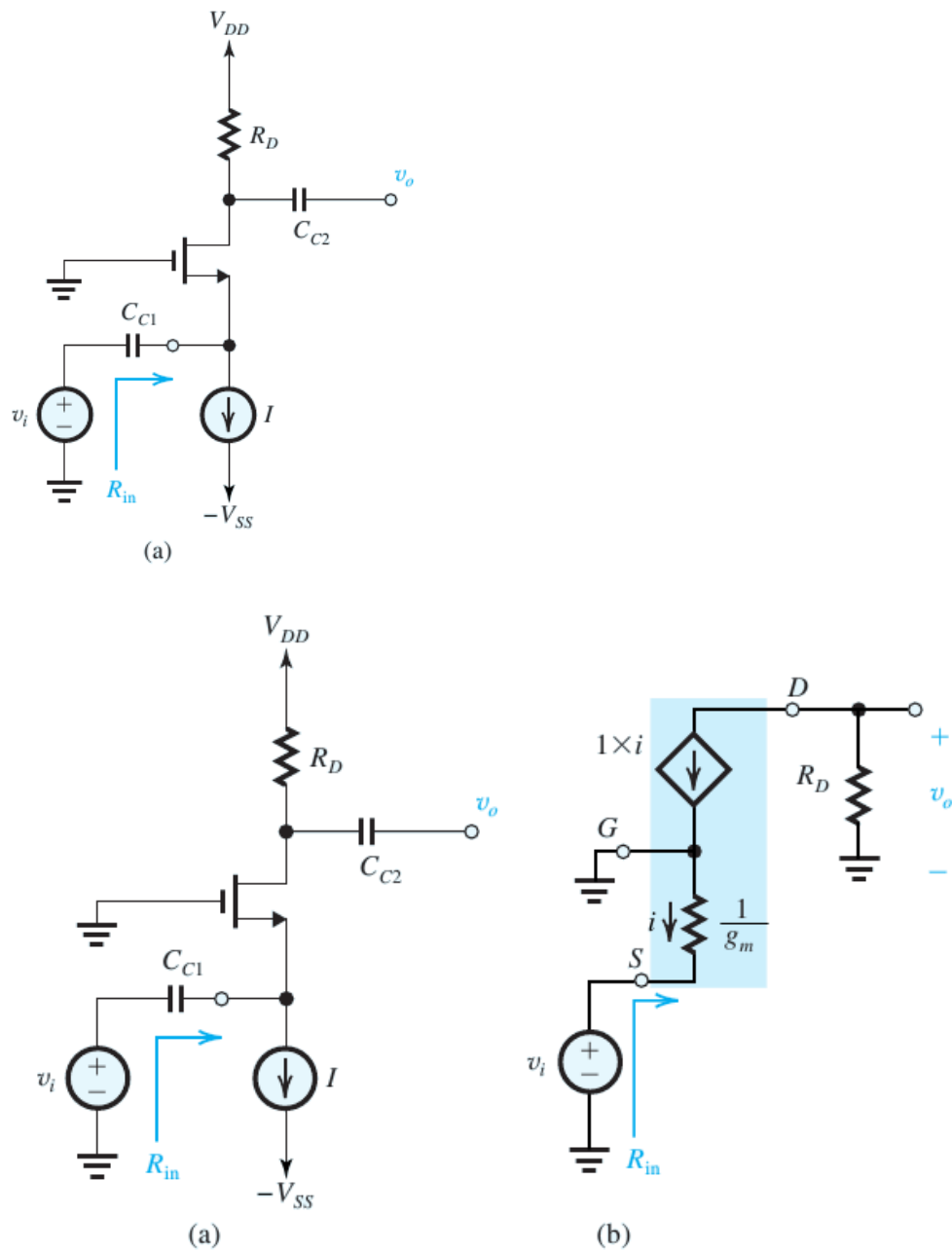


Figure 5.42 (a) Amplifier circuit for Example 5.11; (b) Small-signal equivalent circuit of the amplifier in (a).

- as $\frac{v_{gs}}{i} = \frac{1}{g_m}$ and $v_{gs} = -v_i$
 - $\Rightarrow \frac{-v_i}{i} = \frac{1}{g_m}$
 - and $R_{in} = \frac{v_i}{i} = \frac{v_i}{-i} = \frac{-v_i}{i} = \frac{1}{g_m}$
 - by ohm's law at R_D
 - $v_o = (-i)R_D$
 - As $i = \frac{v_{gs}}{1/g_m} = g_m v_{gs}$
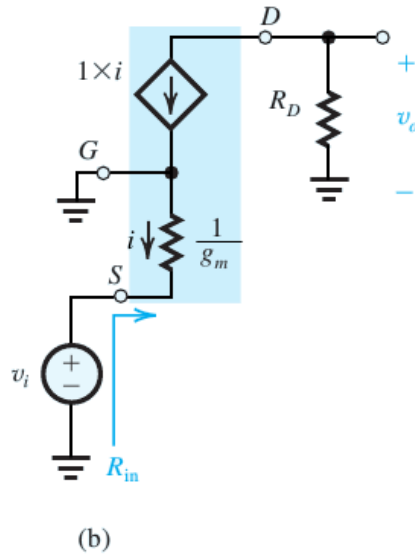
$$\begin{aligned} \blacksquare & \Rightarrow v_o = -g_m v_{gs} R_D \\ \blacksquare & \text{ or } v_o = -g_m (-v_i) R_D \because v_{gs} = -v_i \\ \blacksquare & v_o = g_m v_i R_D \Rightarrow A_v = \frac{v_o}{v_i} = g_m R_D \end{aligned}$$



Basic MOSFET Amplifier Configurations

Basic MOSFET Amplifier Configurations

- we have already determined that
 - almost-linear amplification can be obtained by
 - biasing the MOSFET at a suitable point Q in
 - its saturation region of operation
 - and by keeping the signal v_{gs} small

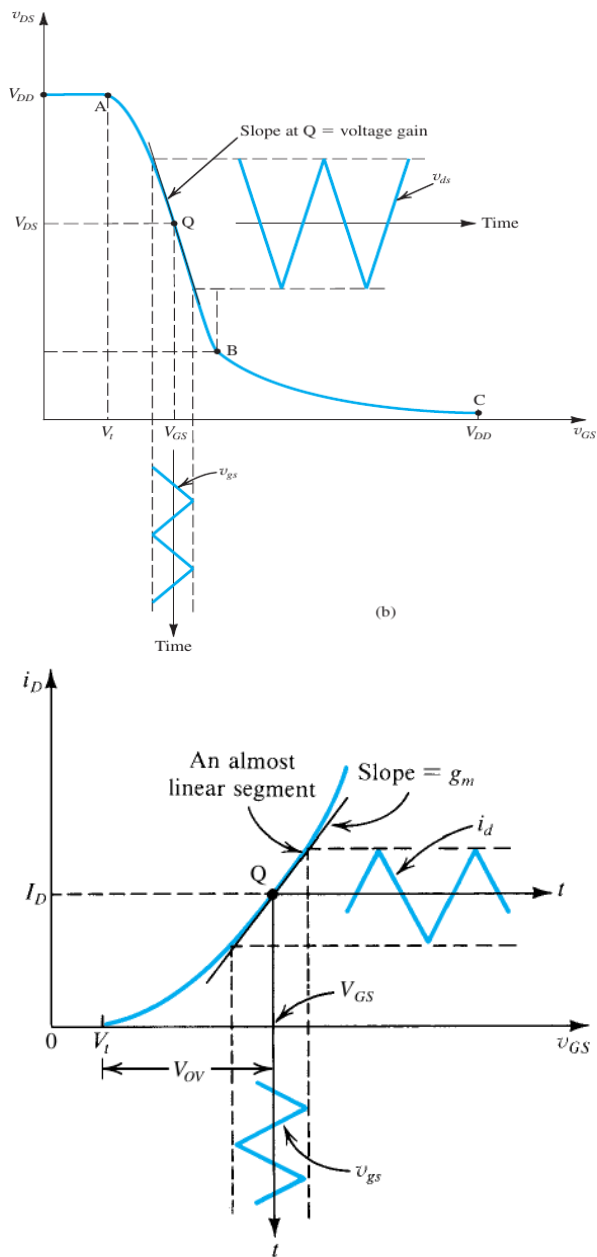


Figure 5.35 Small-signal operation of the MOSFET amplifier.

Basic MOSFET Amplifier Configurations

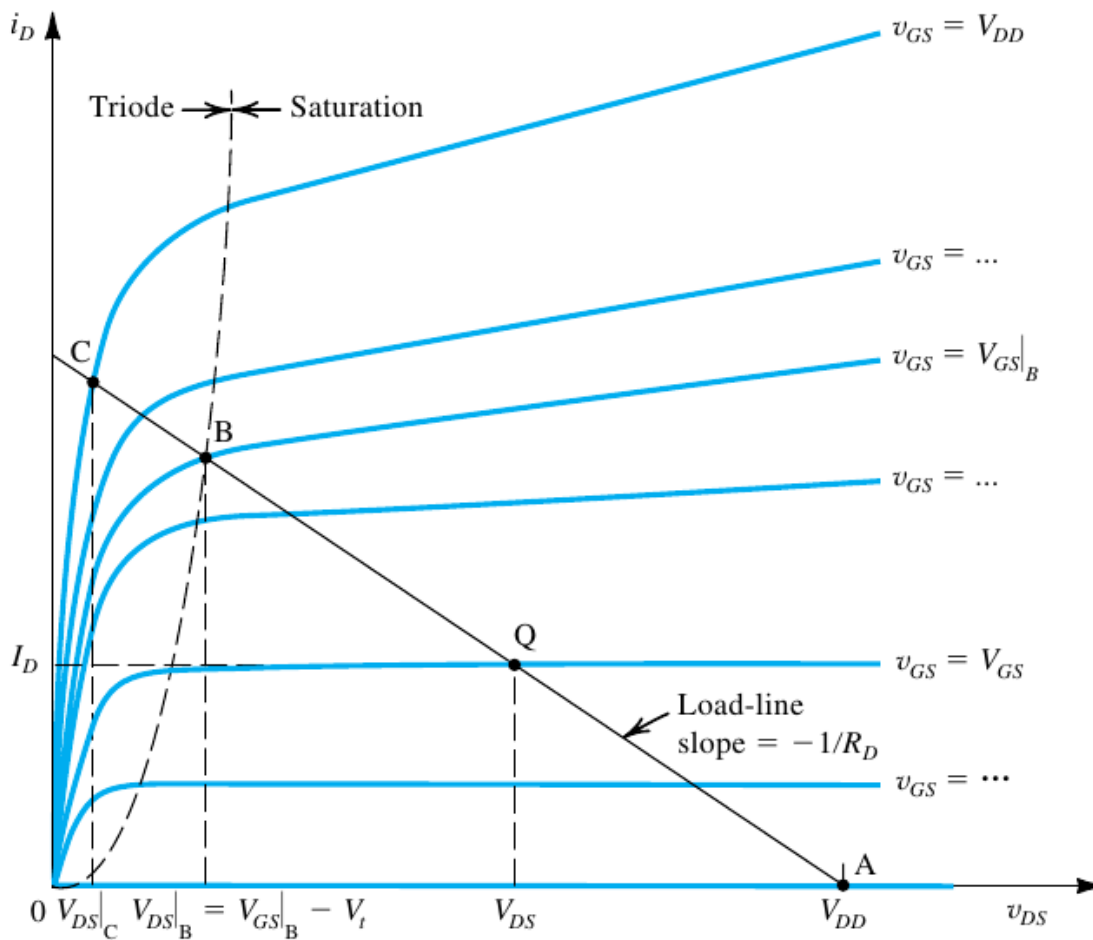


Figure 5.31 Graphical construction to determine the voltage transfer characteristic of the amplifier in Fig. 5.29(a).

- Also when v_{gs} is small, the MOSFET can be replaced by its small-signal circuit model (either hybrid- π model or the T-model)
 - the resultant ac circuit can be used to determine the amplifier parameters like
 - the voltage gain,
 - the input resistance
 - and the output resistance


Table 5.3 Small-Signal Equivalent-Circuit Models for the MOSFET**Small-Signal Parameters****NMOS transistors**

■ Transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$$

■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$

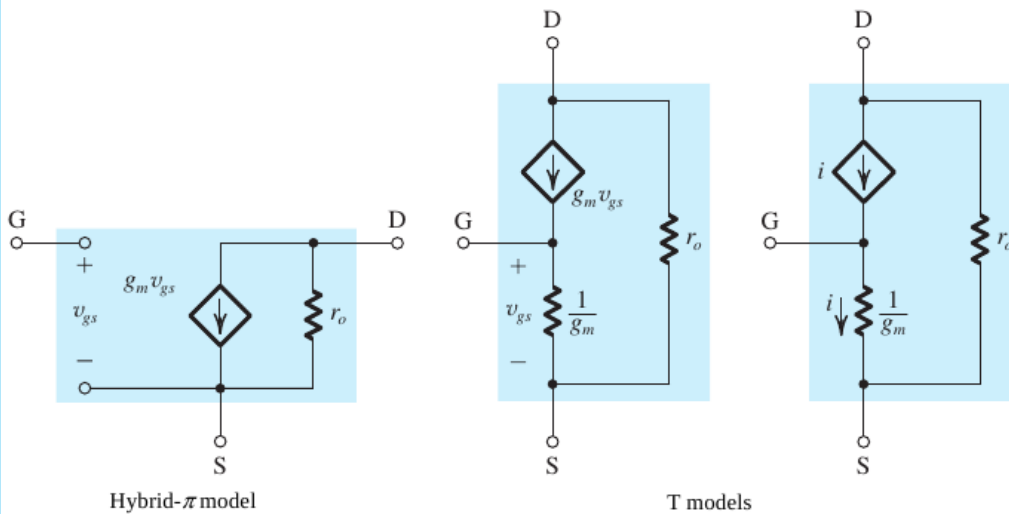PMOS transistorsSame formulas as for NMOS except using $|V_{OV}|$, $|V_A|$, and replacing μ_n with μ_p .**Small-Signal Equivalent Circuit Models****The Three Basic Configurations**

- There are three basic configurations for connecting the MOSFET as an amplifier, namely
 - the Common Source (CS) Amplifier
 - the Common Gate (CG) Amplifier
 - The Common Drain (CD) Amplifier (also called Source Follower)
 - Each of these configurations is obtained by
 - connecting one of the three MOSFET terminals to ground
 - thus creating a two-port network with the grounded terminal
 - being common to the input and output ports
 - The resulting three configurations with biasing arrangement omitted are shown in fig


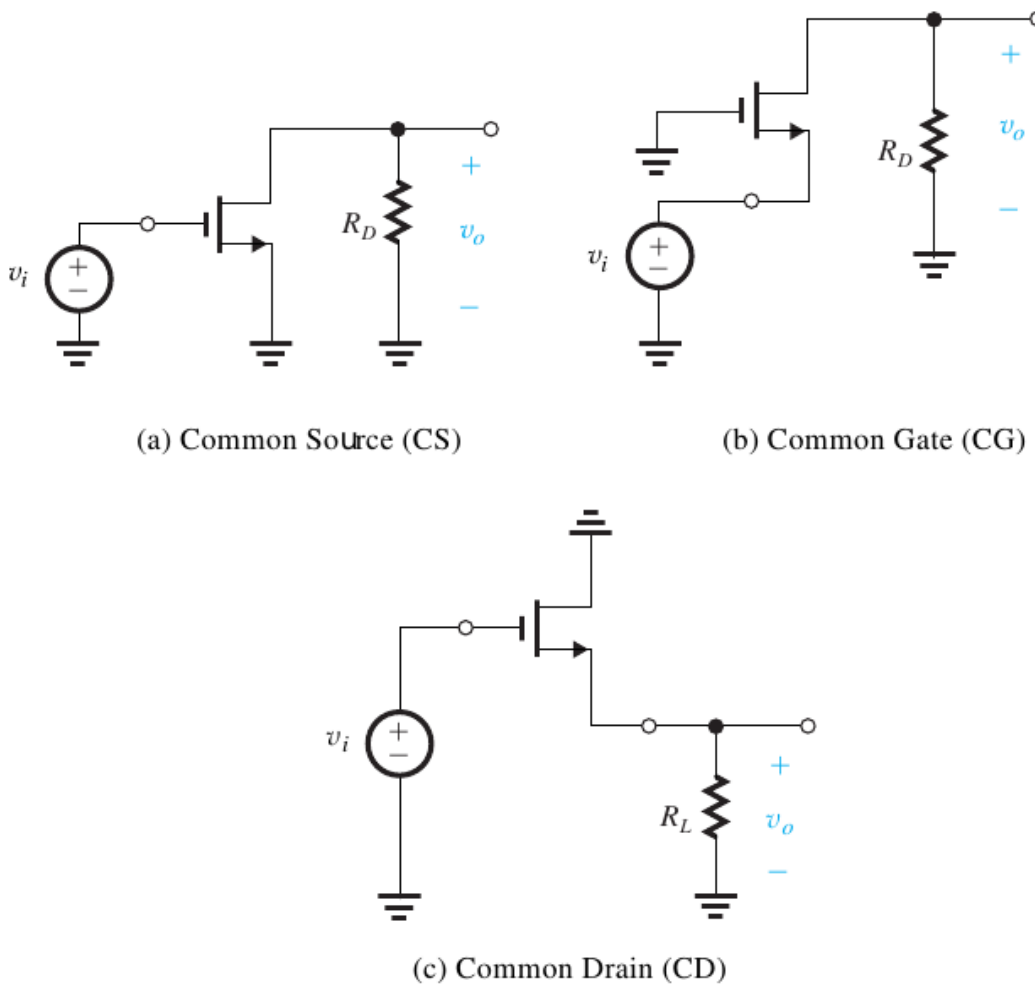


Figure 5.43 The three basic MOSFET amplifier configurations.

Common Source Amplifier

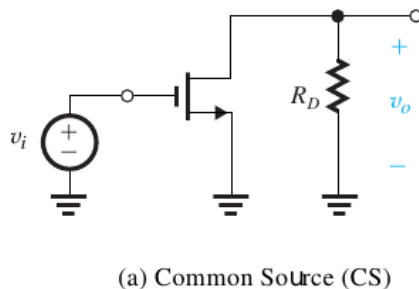
- here the source terminal is connected to ground,
 - the input voltage is applied at the gate (w.r.t ground),
 - the output voltage is taken at the drain (w.r.t ground)



- this configuration is called the grounded source or the common source (CS) amplifier
- Note that dc biasing circuit is not shown in figure

Common Gate Amplifier

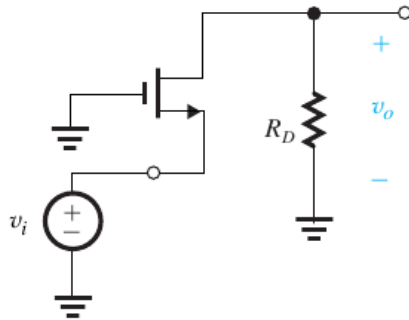- The common gate (CG) or grounded gate amplifier is obtained
 - by connecting the gate to ground,
 - applying the input between the source and ground
 - taking the output v_o between the drain and ground




(b) Common Gate (CG)

- Note that dc biasing circuit is not shown in figure

Common Drain Amplifier

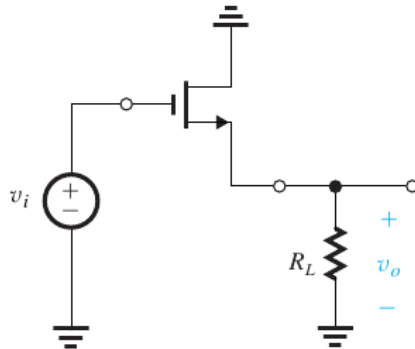- The common drain (CD) or grounded drain amplifier is obtained
 - by connecting the drain terminal to ground,
 - applying the input between the gate and ground
 - taking the output v_o between the source and ground



(c) Common Drain (CD)


- Note that dc biasing circuit is not shown in figure
- the Common Drain amplifier is also called Source Follower

Characterizing Amplifiers


- lets take a look at how to characterize the performance of an amplifier

as a circuit building block

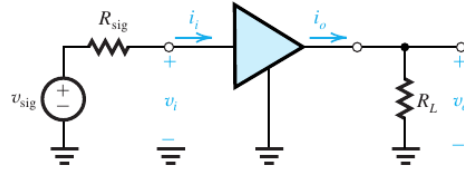- here an amplifier is fed with a signal source
 - having an open-circuit voltage v_{sig} and an internal resistance R_{sig}




- this voltage source (v_{sig} , R_{sig}) can be an actual signal source
 - or in a cascade amplifier, it can be the Thevenin equivalent of the output circuit of the preceeding amplifier.
- the load resistor R_L is connected at the output terminal of the amplifier
 - this R_L can be an actual load resistor
 - or the input resistance of a succeeding amplifier stage in a cascade amplifier
- The amplifier block can be replaced by its equivalent circuit model

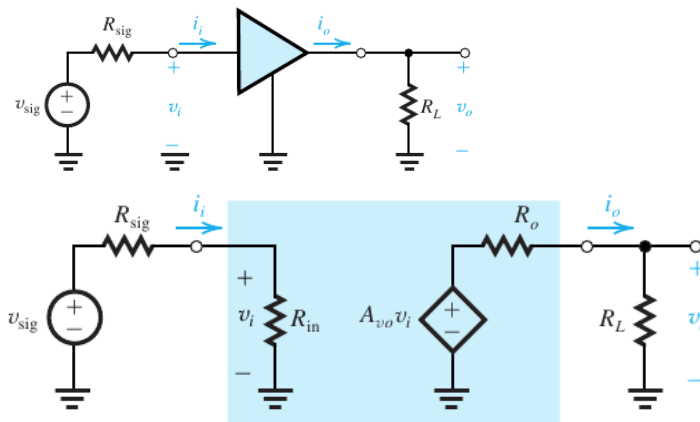

(b)


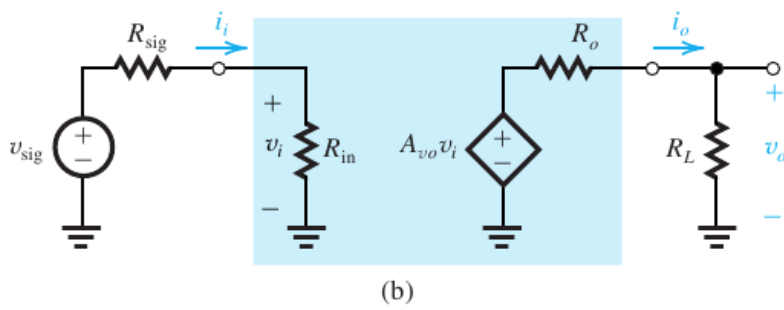
- the input resistance R_{in}
 - indicate the loading effect of the amplifier input on the signal source
 - and is given as $R_{in} = \frac{v_i}{i_i}$
- by voltage divider rule
 - $v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$



- $v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$

- A_{vo} is the open-circuit voltage gain and is defined as

- $A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L = \infty}$

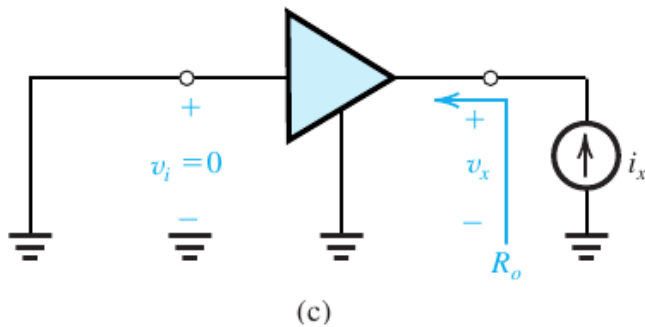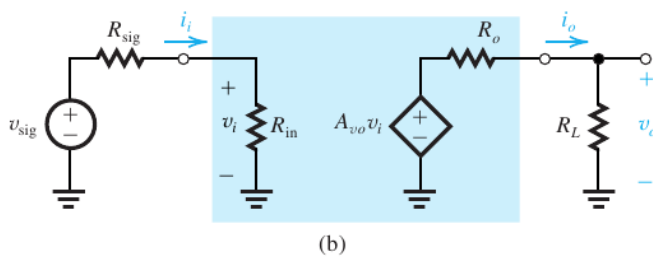


- the 3rd parameter that is essential to characterize an amplifier is the output resistance R_o

- R_o is the resistance seen looking back into the amplifier output terminal with v_i set to zero

- $\Rightarrow R_o = \frac{v_x}{i_x}$

- Note that the controlled source $A_{vo} v_i$ and the output resistance R_o

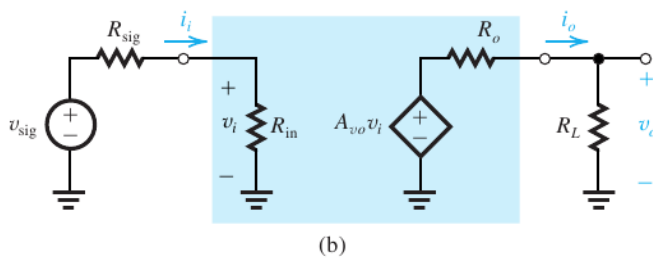- represent the Thevenin equivalent of the amplifier output circuit.



- by voltage divider

- the output voltage v_o can be given as

- $v_o = \frac{R_L}{R_L + R_o} (A_{vo} v_i) \Rightarrow \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o}$

- thus the voltage gain of the amplifier is

- $A_v = \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o}$

- the overall voltage gain is

- $G_v = \frac{v_o}{v_{sig}} = A_{vo} \frac{R_L}{R_L + R_o} \frac{v_i}{v_{sig}}$

- $G_v = A_{vo} \frac{R_L}{R_L + R_o} \frac{R_{in}}{R_{in} + R_{sig}} \because v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$
