

Lecture 7b


EE-215 Electronic Devices and Circuits

Asst Prof Muhammad Anis Ch

Basic MOSFET Amplifier Configurations

The Common-Source (CS) Amplifier

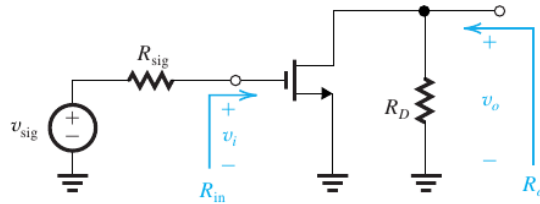- is the most widely used MOS amplifier configuration



- (a)
- Note that, here the biasing arrangement is not shown (the circuit in fig is the ac equivalent circuit)
- the signal source has an internal resistance of R_{sig} and open circuit voltage of v_{sig}
- let's analyze this circuit to determine R_{in} , A_{vo} , R_o and G_v
- Note that R_D is part of the amplifier circuit, and when a load resistance R_L is connected

- to the amplifier output, it appears in parallel with R_D

- replacing MOSFET with its hybrid- π model


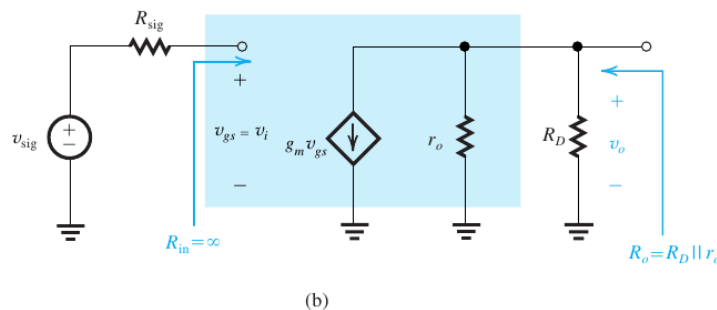
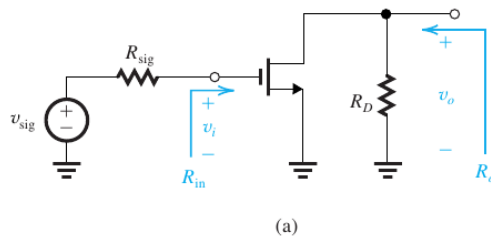


Figure 5.45 (a) Common-source amplifier fed with a signal v_{sig} from a generator with a resistance R_{sig} . The

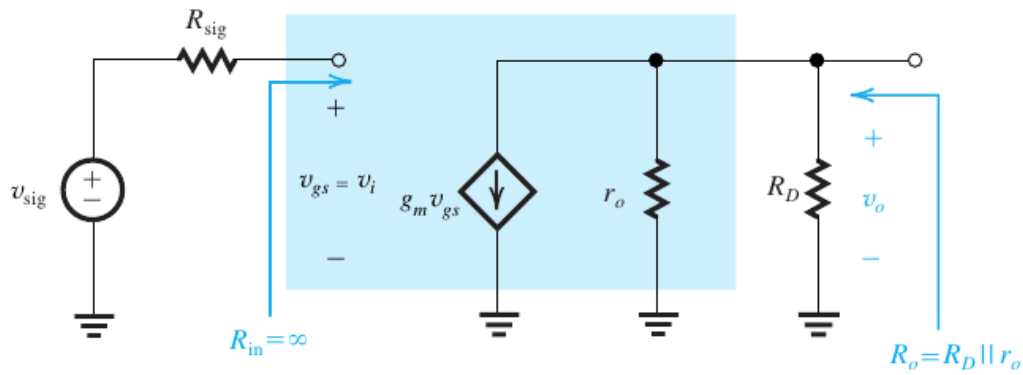- bias circuit is omitted. (b) The common-source amplifier with the MOSFET replaced with its hybrid- π model.




(b)

- this equivalent circuit can be used to determine the characteristic parameters (R_{in} , A_{vo} , R_o) of the amplifier
- from the fig

■ as gate current is zero $\Rightarrow$ input resistance $= R_{in} = \infty$

◦ by KCL $\Rightarrow g_m v_{gs} + \frac{v_o}{r_o \parallel R_D} = 0$

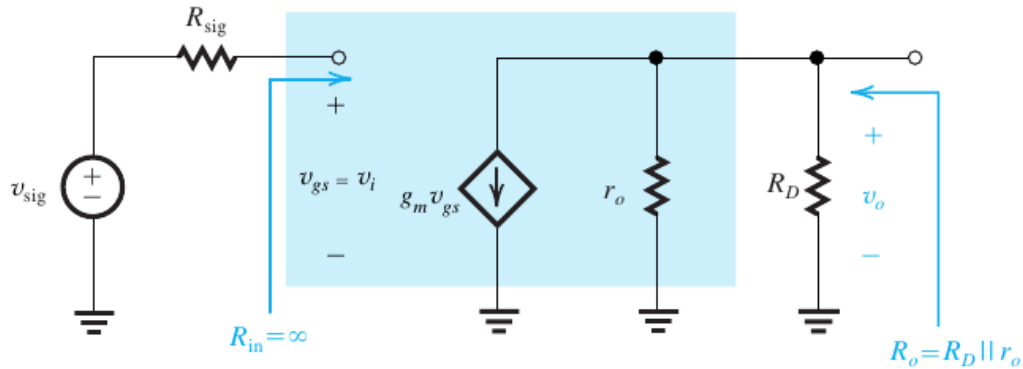■ $v_o = -g_m v_{gs} (r_o \parallel R_D) \Rightarrow \frac{v_o}{v_{gs}} = -g_m (r_o \parallel R_D)$




(b)

◦ $\frac{v_o}{v_{gs}} = -g_m (r_o \parallel R_D)$

◦ here $v_i = v_{gs} \Rightarrow A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left. \frac{v_o}{v_{gs}} \right|_{R_L=\infty} = -g_m (r_o \parallel R_D)$

◦ if the channel length modulation can be ignored $r_o \rightarrow \infty$ ($r_o > R_D$)

■ $\Rightarrow A_{vo} \approx -g_m R_D$

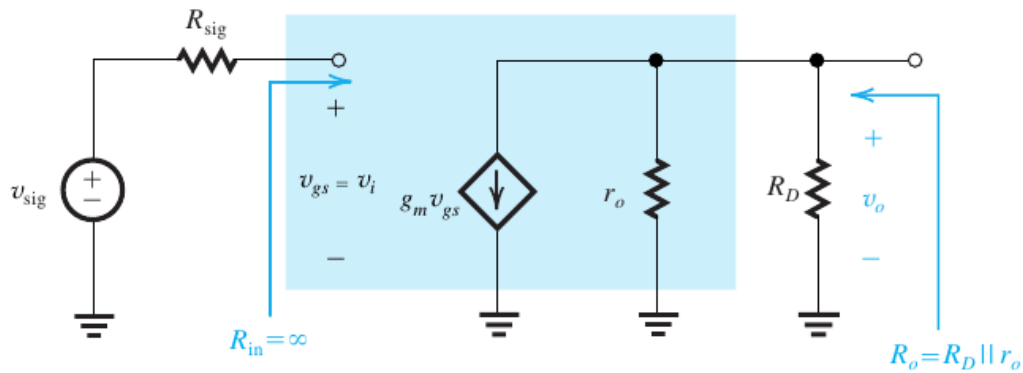


(b)

- Now the output resistance R_o is the resistance seen looking into the output terminal with v_i set to zero

$$\begin{aligned} \blacksquare v_i = 0 &\Rightarrow v_{gs} = 0 \Rightarrow g_m v_{gs} = 0 \\ \blacksquare &\Rightarrow R_o = R_D \parallel r_o \end{aligned}$$

- thus for CS amplifier
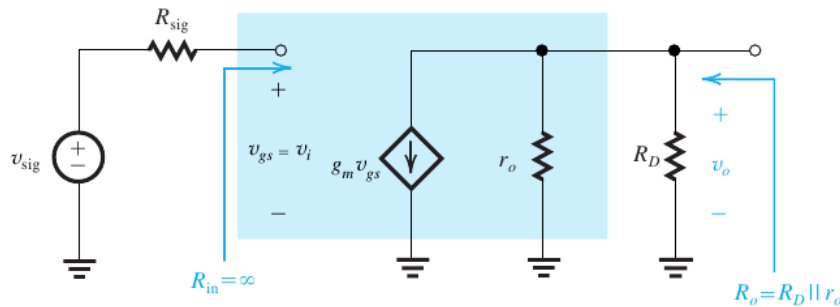
$$\blacksquare R_{in} = \infty, R_o = R_D \parallel r_o, A_{vo} = -g_m (R_D \parallel r_o)$$



(b)

- now the overall voltage gain G_v can be determined as follows

$$\blacksquare G_v = \frac{v_o}{v_{sig}}$$


- As $R_{in} = \infty \Rightarrow v_{sig} = v_i = v_{gs}$

$$\Rightarrow G_v = \frac{v_o}{v_{sig}} = \frac{v_o}{v_i} = A_v$$

- Note that A_v, G_v are calculated with load resistor R_L connected $\Rightarrow v_o = (-g_m v_{gs})(R_D \parallel r_o \parallel R_L)$


$$\blacksquare \frac{v_o}{v_{gs}} = -g_m (R_D \parallel r_o \parallel R_L) = \frac{v_o}{v_i} = G_v = A_v \because v_i = v_{gs}$$

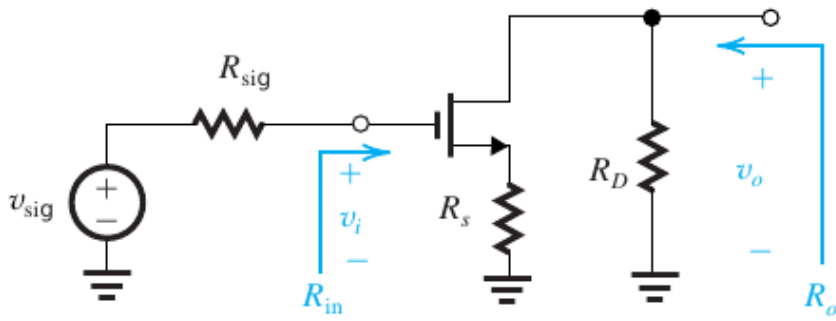The Common-Source (CS) Amplifier with a Source Resistance




(a)

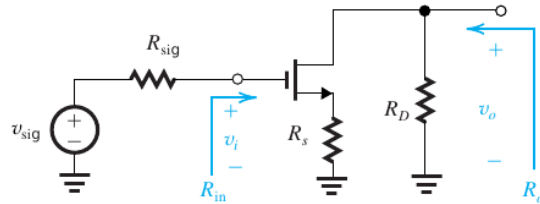- here we have placed a resistance R_s in the source lead of the common-source amplifier
 - Assuming $\lambda = 0$ i.e. ignoring channel length modulation
- the small-signal equivalent circuit can be drawn as (for $\lambda = 0$)




(a)

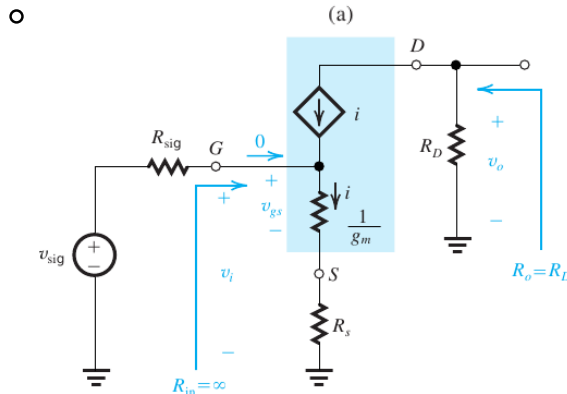


(b)

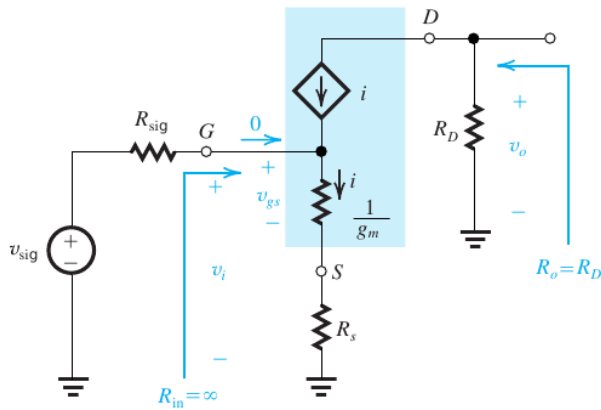- here T-model is preferred over the π model, because it makes the analysis somewhat simple
 - In general, whenever a resistance is connected in the source lead, the T model is preferred.



(b)

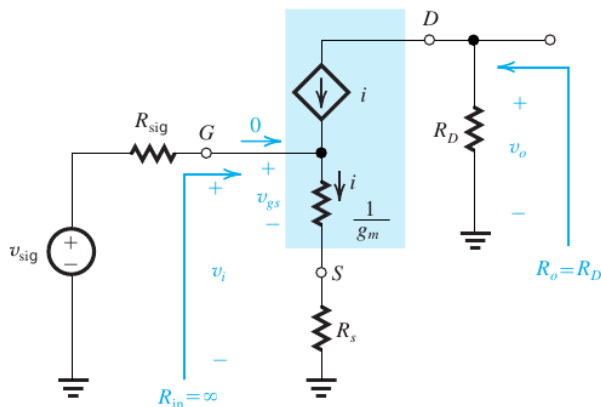- As a consequence of the T-model, R_s appears in series with the resistance $1/g_m$
 - as gate current is zero $\Rightarrow R_{in} = \infty \Rightarrow v_i = v_{sig}$
 - here only a fraction of v_i appears between gate and source as v_{gs}
 - by voltage divider $\Rightarrow v_{gs} = \frac{(1/g_m)}{(1/g_m) + R_s} v_i = \frac{1}{1 + g_m R_s} v_i$




(b)

- $v_{gs} = \frac{(1/g_m)}{(1/g_m) + R_s} v_i = \frac{1}{1 + g_m R_s} v_i$
 - thus the value of R_s can be used to control the magnitude of the signal v_{gs}
 - and thereby ensure that v_{gs} doesnot become too large to cause
 - unacceptably high non-linear distortion
 - Another benefit is that R_s extends the useful bandwidth of the amplifier
- by ohm's law,
 - $v_o = -i R_D$
 - As $1/g_m$ and R_s are in series, the current i in the source lead

can be given as

$$\blacksquare i = \frac{v_i}{1/g_m + R_s} = \left(\frac{g_m}{1 + g_m R_s} \right) v_i$$
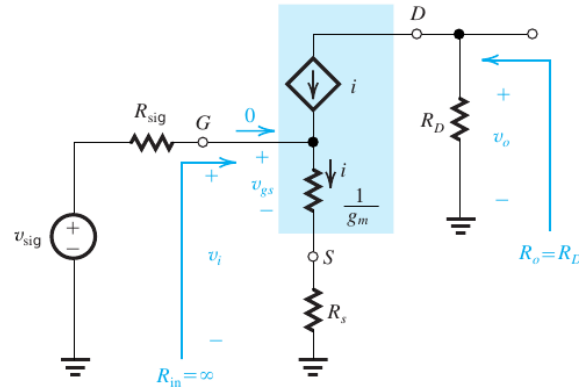
$$\blacksquare \Rightarrow v_o = -i R_D = -\left(\frac{g_m}{1 + g_m R_s} \right) v_i R_D$$



(b)

◦ the voltage gain, $A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = -\left(\frac{g_m}{1 + g_m R_s} \right) R_D = \frac{-g_m R_D}{1 + g_m R_s}$


◦ $\Rightarrow$ the resistance R_s reduces the voltage gain by the factor $(1 + g_m R_s)$

• $A_{vo} = -\frac{g_m R_D}{1 + g_m R_s}$

◦ divide numerator and denominator by g_m on R.H.S

◦ $A_{vo} = -\frac{R_D}{\frac{1}{g_m} + R_s}$

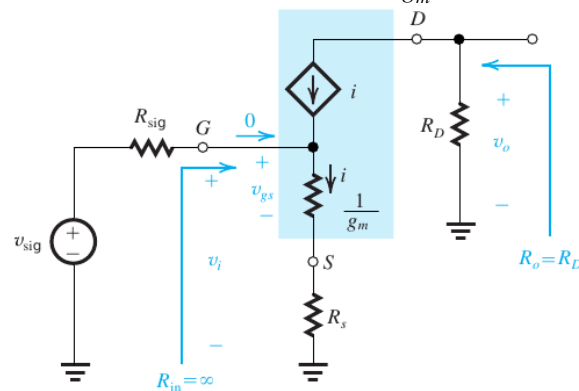$\blacksquare \Rightarrow$ the voltage gain between gate and the drain is equal to the ratio of the total resistance in the drain (R_D) to the total resistance in the source ($\frac{1}{g_m} + R_s$)




(b)


◦ i.e.

$$\text{Voltage gain from gate to drain} = -\frac{\text{Total Resistance in drain}}{\text{Total Resistance in source}} = -\frac{R_D}{\frac{1}{g_m} + R_s}$$

- Note that setting $R_s = 0$ gives A_{vo} of the CS amp = $-\frac{R_D}{(1/g_m)}$
- the output resistance R_o can be determined by placing a test source at the drain
 - and by setting $v_i = 0 \Rightarrow v_{gs} = 0 \Rightarrow i = g_m v_{gs} = 0$
 - $i = 0 \Rightarrow R_o = R_D$
 - now when R_L is connected at the output, A_v can be given as
 - $A_v = A_{vo} \frac{R_L}{R_L + R_o}$
 - As $A_{vo} = -\frac{g_m R_D}{1 + g_m R_s}$, $R_o = R_D$

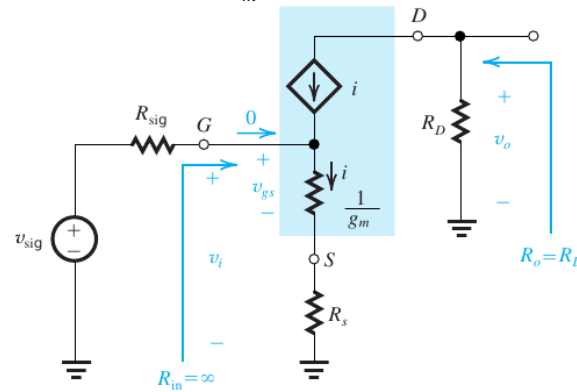


- $\Rightarrow A_v = A_{vo} \frac{R_L}{R_L + R_o} = \left(-\frac{g_m R_D}{1 + g_m R_s} \right) \frac{R_L}{R_L + R_D}$
- $A_v = \left(-\frac{g_m R_D}{1 + g_m R_s} \right) \frac{R_L}{R_L + R_D} = \left(-\frac{g_m}{1 + g_m R_s} \right) \frac{R_D R_L}{R_L + R_D}$
 - $A_v = \left(-\frac{g_m}{1 + g_m R_s} \right) \left(\frac{1}{\frac{1}{R_D} + \frac{1}{R_L}} \right) = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$
 - $A_v = -\frac{R_D \parallel R_L}{(1/g_m) + R_s}$
 - Note that $-A_v$ is the ratio of the total resistance in drain to the total resistance in source
 - As R_{in} is infinite $\Rightarrow v_i = v_{sig}$

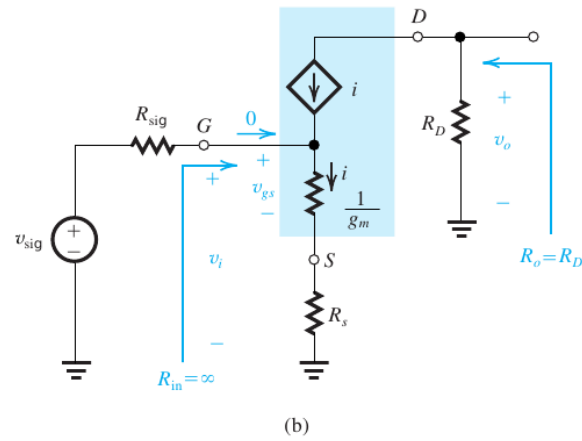

◦ and the overall voltage gain is $G_v = \frac{v_o}{v_{sig}} = \frac{v_o}{v_i} = A_v$

The Common-Gate (CG) Amplifier

- here common-gate amplifier is shown
 - Note that the biasing circuit is not shown in figure
 - the amplifier is fed with a signal source characterized by v_{sig} and R_{sig}
 - Note that R_{sig} appears in series with the source
 - $\Rightarrow$ it is more convenient to use the T model rather than the π model

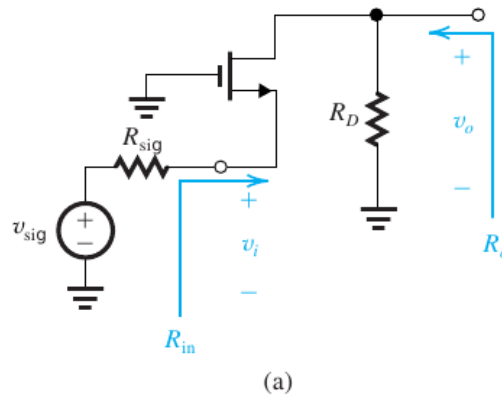


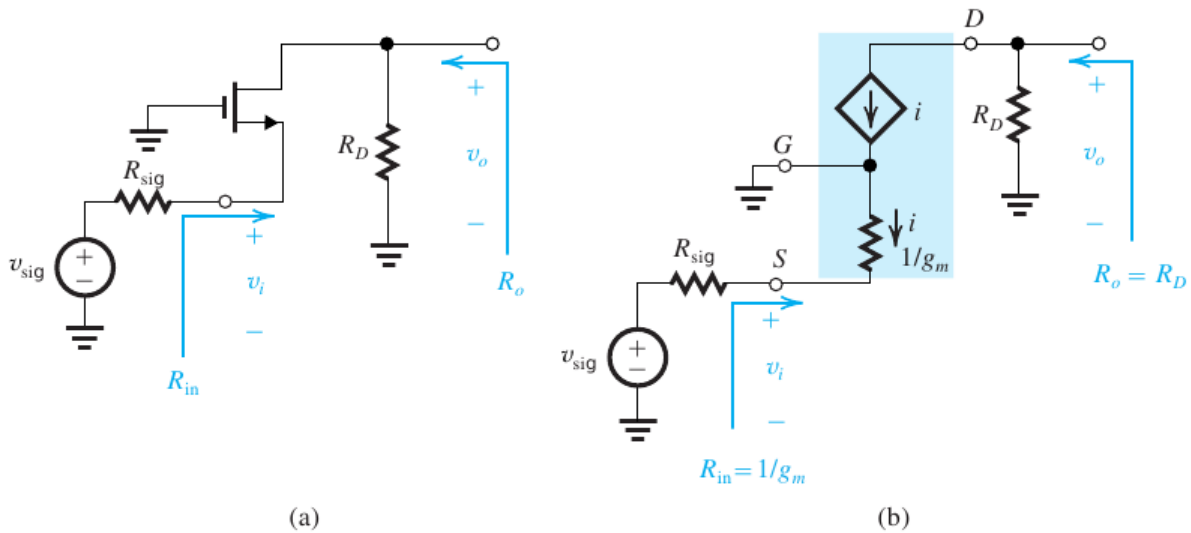


Figure 5.48 (a) Common-gate (CG) amplifier with bias arrangement omitted. (b) Equivalent circuit of the CG amplifier with the MOSFET replaced with its T model.

- here channel length modulation is ignored
- the input resistance R_{in} can be given as $R_{in} = \frac{1}{g_m}$
 - as R_{in} is the resistance looking into the source and the gate is grounded
 - typically $1/g_m$ is a few hundred ohms
 - $\Rightarrow$ the CG amplifier has a low input resistance
 - by ohm's law
 - $v_o = (-i)R_D$,
 - where i is also the source current
 - i.e. $i = \frac{0-v_i}{1/g_m} = -v_i g_m$

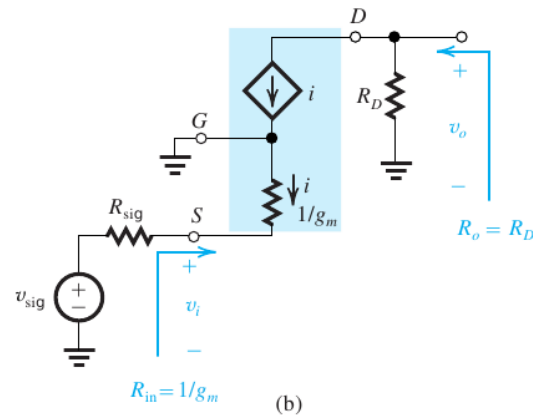


$$\circ \Rightarrow v_o = v_i g_m R_D \Rightarrow A_{vo} = \frac{v_o}{v_i} = g_m R_D = \frac{R_D}{1/g_m}$$

- The output resistance of the CG amplifier is
 - $R_o = R_D$
 - the gain A_v is

$$\blacksquare A_v = \frac{v_o}{v_i} = g_m (R_D \parallel R_L)$$
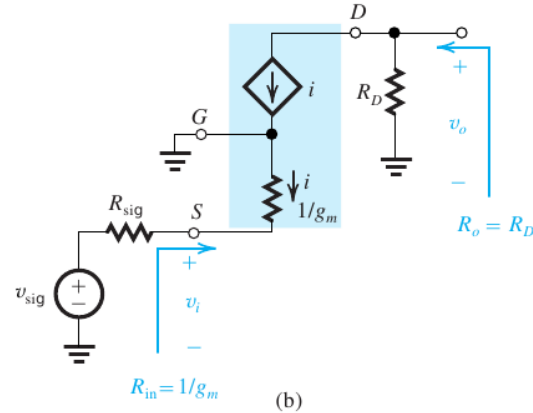
$$\blacksquare \because A_{vo} = g_m R_D \text{ and as } R_L \text{ is in parallel with } R_D$$



- To determine the overall gain G_v

- first by voltage divider

$$\blacksquare v_i = \frac{(1/g_m)}{(1/g_m) + R_{sig}} v_{sig} = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$$


$$\blacksquare G_v = \frac{v_o}{v_{sig}} = \frac{v_o}{v_i} \frac{v_i}{v_{sig}}$$

$$\blacksquare G_v = \frac{v_o}{v_i} \frac{v_i}{v_{sig}} = A_v \frac{v_i}{v_{sig}} = A_v \frac{(1/g_m)}{(1/g_m) + R_{sig}}$$

$$\blacksquare \because A_v = g_m (R_D \parallel R_L)$$

$$\blacksquare G_v = g_m (R_D \parallel R_L) \frac{(1/g_m)}{(1/g_m) + R_{sig}}$$
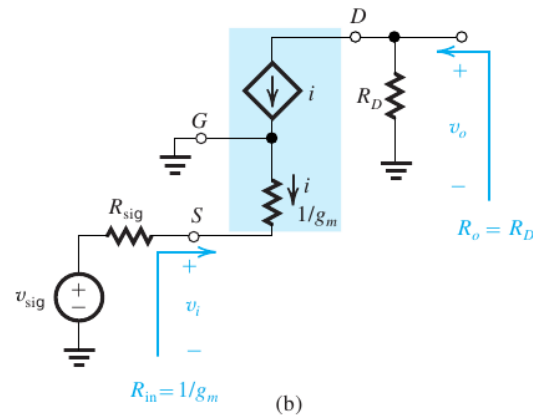
$$\blacksquare G_v = \frac{R_D \parallel R_L}{(1/g_m) + R_{sig}}$$



$$\bullet G_v = \frac{R_D \parallel R_L}{(1/g_m) + R_{sig}}$$

- Note that the overall voltage gain is simply the ratio of


- the total resistance in the drain circuit
- to the total resistance in the source circuit

- CG amplifier has excellent frequency response and can be used to
 - amplify high-frequency signals that originate from sources
 - with relatively low resistances


The Common-Drain Amplifier or Source Follower

- The common-drain amplifier is more commonly known as the source follower
 - A common application of a CD amplifier is as a voltage buffer


The need for Voltage Buffers

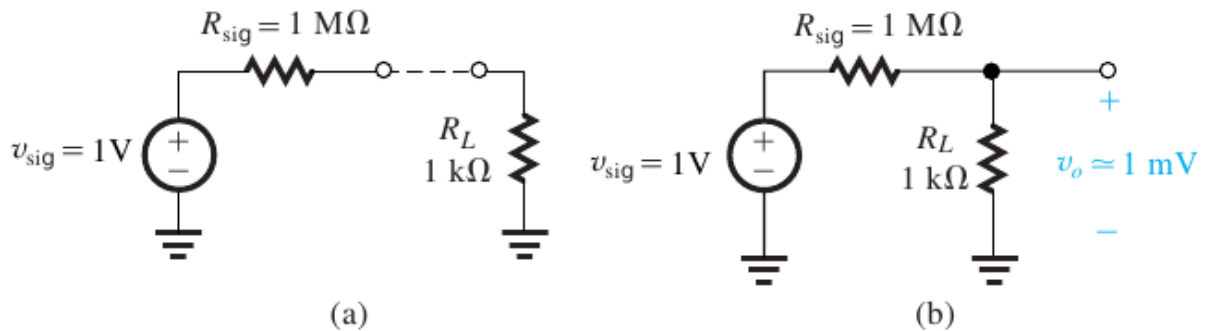

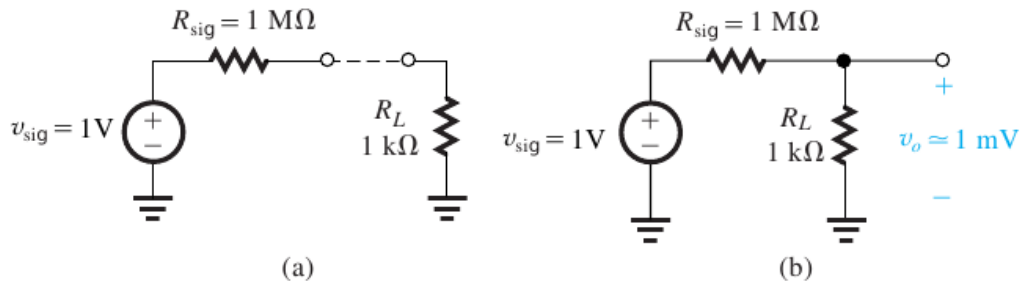
- consider the situation shown in fig
 - here a signal source with open-circuit voltage of $v_{sig} = 1V \text{ peak}$
 - and internal resistance of $1M\Omega$ is to be connected to a $1k\Omega$ load resistance



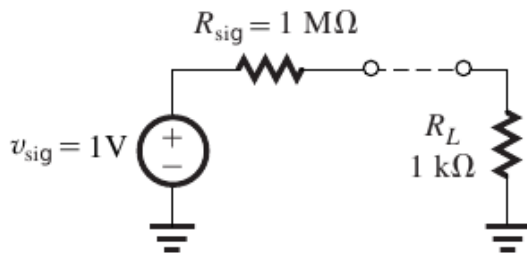- connecting the source to the load directly will result in
 - severe attenuation of the signal
 - i.e. the voltage appearing across the load is
 - $v_o = \frac{R_L}{R_L + R_{sig}} v_{sig} = \frac{1k}{1k + 1M} v_{sig}$
 - As $v_{sig} = 1V \Rightarrow v_o = \frac{1k}{1k + 1M} v_{sig} = 0.999mV \approx 1mV$
 - thus for $v_{sig} = 1V \text{ peak}$, output voltage is only $v_o = 1mV \text{ peak}$




(a)

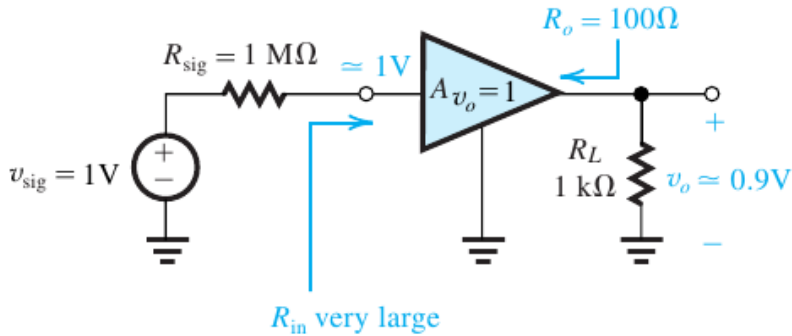


(c)

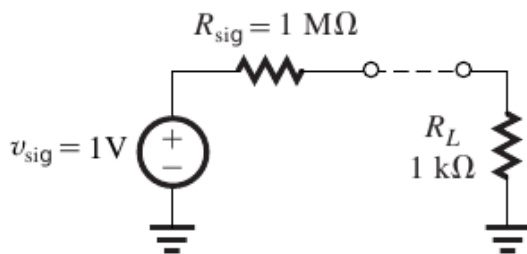- now suppose, we have an amplifier as shown in fig
 - this amplifier is used to connect the source to the load
 - this amplifier has a unity voltage gain
 - (here our signal is already of sufficient strength and increase in its amplitude is not required)



(a)

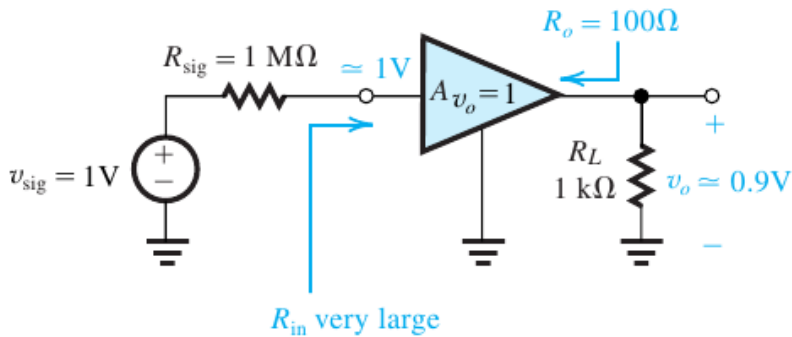


(c)

- this amplifier has a very large input resistance (R_{in} is very large)


$$\circ \Rightarrow v_i \approx v_{sig}$$

- the amplifier has an output resistance of

$$\blacksquare R_o = 100\Omega$$

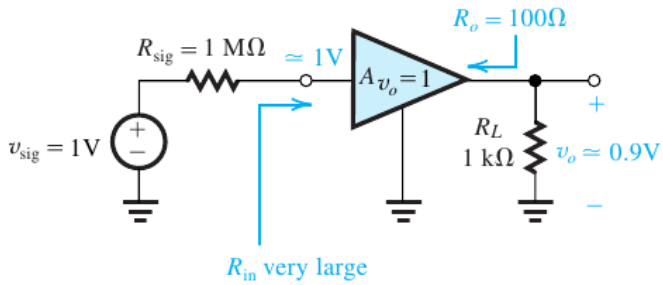

(c)

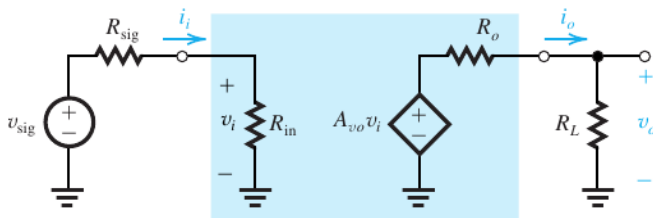

(b)

- here $R_o = 100\Omega$, $R_L = 1k\Omega$, $v_i \approx v_{sig}$, $A_{vo} = 1$

- by voltage divider

$$\blacksquare v_o = \frac{R_L}{R_L + R_o} A_{vo} v_i = \frac{1k}{1k + 100} (1) v_{sig} = 0.9V$$

- $\Rightarrow$ 90% of the input signal appears at the output


- such an amplifier circuit with $A_{vo} = 1$, $R_{in} \rightarrow \infty$ and $R_{out} \rightarrow 0$ is called a voltage buffer

The Common-Drain Amplifier or Source Follower

- The source follower can be used to implement the unity gain buffer amplifier



- the CD amplifier with the bias circuit omitted is shown here

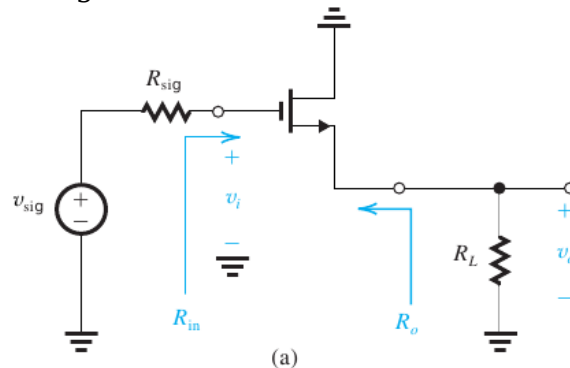- a signal generator (v_{sig} , R_{sig}) is applied between the gate and ground
- a load resistance R_L is connected between the source terminal and ground




(a)

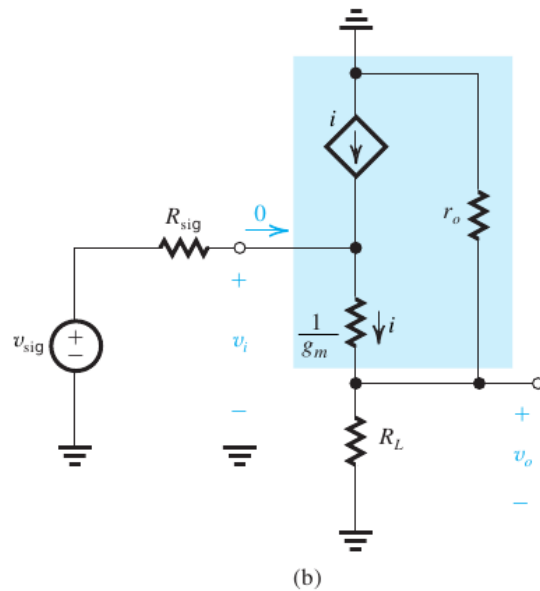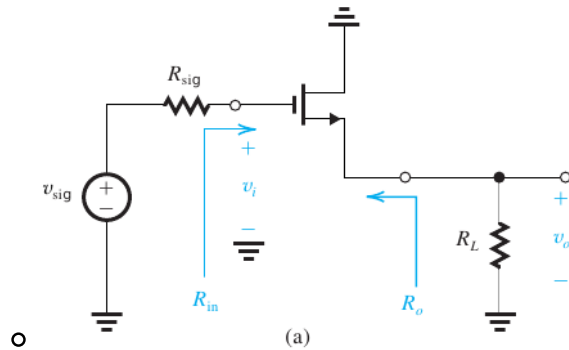- As R_L is connected to the source terminal, it is more convenient to use the T-model rather than the hybrid- π model
- here r_o appears in parallel with R_L . so channel length modulation effect can easily be incorporated.



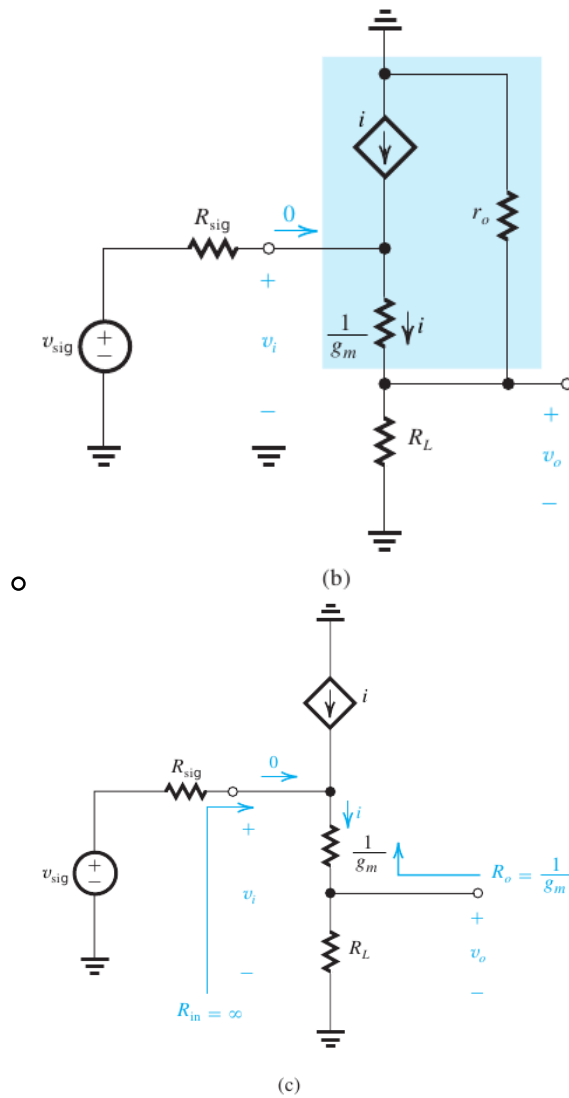- if we ignore channel length modulation $\Rightarrow r_o = \infty$



• from figure

◦ $R_{in} = \infty$

■ as no current flows in to the gate terminal


■ $\Rightarrow v_i = v_{sig}$

■ by voltage divider

$$\blacksquare \frac{v_o}{v_i} = \frac{R_L}{R_L + (1/g_m)} = A_v$$

■ and A_{vo} can be given as

$$\blacksquare A_{vo} = \left. \frac{v_o}{v_i} \right|_{R_L=\infty} = \left. \frac{R_L}{R_L + (1/g_m)} \right|_{R_L=\infty}$$

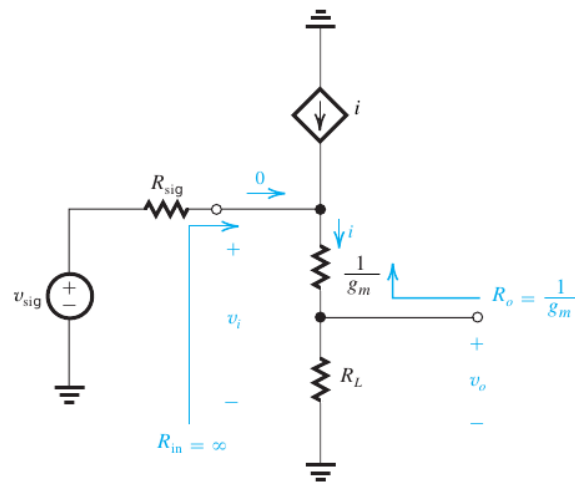

(c)

$$A_{vo} = \left. \frac{1}{1 + \frac{1}{g_m} \frac{1}{R_L}} \right|_{R_L = \infty} = \frac{1}{1+0} = 1$$

- the output resistance R_o is determined by setting $v_i = 0$ and $R_L = \infty$


◦ $\Rightarrow v_i = 0 \Rightarrow$ the gate terminal is grounded

$$\Rightarrow R_o = \frac{1}{g_m}$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{v_o}{v_i} \because v_i = v_{sig} \text{ because of infinite } R_{in}$$

$$G_v = \frac{v_o}{v_i} = A_v = \frac{R_L}{R_L + (1/g_m)}$$

■ thus G_v will be lower than unity

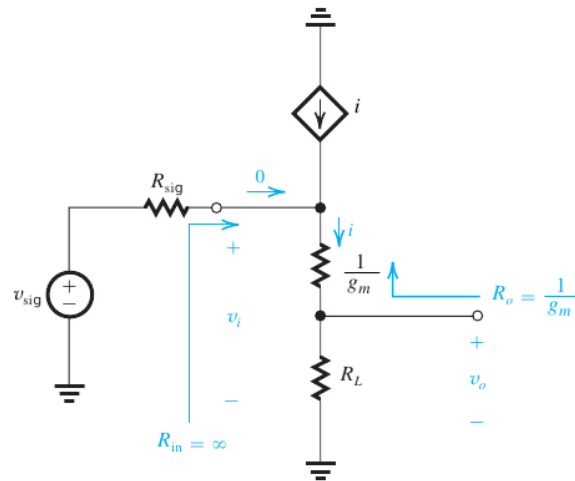

(c)


◦ however, as $1/g_m$ is usually a small value

■ $\Rightarrow$ voltage gain will be close to unity i.e $G_v = A_v \approx 1$

- $G_v = \frac{v_o}{v_i} = A_v \approx 1$ and $A_{vo} = 1$

◦ $\Rightarrow$ the voltage at the source terminal will follow that at the input,

hence the name source follower

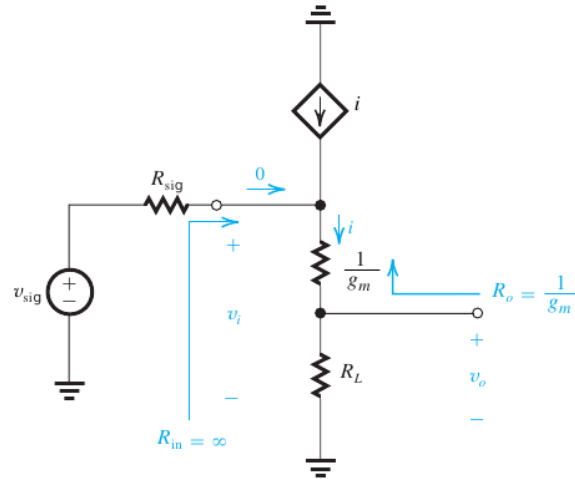

(c)

- thus the source follower has $R_{in} = \infty$, $R_o = \frac{1}{g_m}$ (a small value) and $A_{vo} = 1$, $A_v = G_v \approx 1$
- $\Rightarrow$ the source follower is ideally suited for implementing the unity gain voltage buffer.

Table 5.4 Characteristics of MOSFET Amplifiers

Amplifier type	Characteristics ^{a, b}				
	R_{in}	A_{vo}	R_o	A_v	G_v
Common source (Fig. 5.45)	∞	$-g_m R_D$	R_D	$-g_m (R_D \parallel R_L)$	$-g_m (R_D \parallel R_L)$
Common source with R_s (Fig. 5.47)	∞	$-\frac{g_m R_D}{1 + g_m R_s}$	R_D	$-\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$ $-\frac{R_D \parallel R_L}{1/g_m + R_s}$	$-\frac{g_m (R_D \parallel R_L)}{1 + g_m R_s}$ $-\frac{R_D \parallel R_L}{1/g_m + R_s}$
Common gate (Fig. 5.48)	$\frac{1}{g_m}$	$g_m R_D$	R_D	$g_m (R_D \parallel R_L)$	$\frac{R_D \parallel R_L}{R_{sig} + 1/g_m}$
Source follower (Fig. 5.50)	∞	1	$\frac{1}{g_m}$	$\frac{R_L}{R_L + 1/g_m}$	$\frac{R_L}{R_L + 1/g_m}$

^a For the interpretation of R_{in} , A_{vo} , and R_o , refer to Fig. 5.44(b).

^b The MOSFET output resistance r_o has been neglected, as is permitted in the discrete-circuit amplifiers studied in this chapter. For IC amplifiers, r_o must always be taken into account.