

Number Representation and
Arithmetic Circuits:
Signed Numbers, Binary Adders
and Subtractors

Octal and hexadecimal numbers

- Positional notation can be used for any radix (base). If the radix is r , then the number $K = k_{n-1}k_{n-2} \dots k_1k_0$ has the value

$$V(K) = \sum_{i=0}^{n-1} k_i \times r^i$$

- Numbers with radix-8 are called **octal** and numbers with radix-16 are called **hexadecimal** (or hex)
 - For octal, digit values range from 0 to 7
 - For hex, digital values range from 0-9 and A-F

Numbers in different systems

Decimal	Binary	Octal	Hex
0	0000	0	0
1	0001	1	1
2	0010	2	2
3	0011	3	3
4	0100	4	4
5	0101	5	5
6	0110	6	6
7	0111	7	7

Decimal	Binary	Octal	Hex
8	1000	10	8
9	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F

Binary to hex or octal conversion

- Group binary digits into groups of four and assign each group a hexadecimal digit.

0110	1011	0111
6	B	7

- Binary-to-octal:

011	010	110	111
3	2	6	7

- Hexadecimal-to-binary:


A	1	9
1010	0001	1001

- Octal-to-binary:


5	0	3	1
101	000	011	001

Unsigned number addition

 - Addition of two 1-bit numbers gives four possible combinations



x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Unsigned number addition

- Larger numbers have more bits involved
 - There is still the need to add each pair of bits
 - But, for each bit position i , the addition operation may include a **carry-in** from bit position $i-1$

$X = x_4x_3x_2x_1x_0$	0 1 1 1 1	$(15)_{10}$
$Y = y_4y_3y_2y_1y_0$	0 1 0 1 0	$(10)_{10}$
	1 1 1 0	Generated carries
$S = s_4s_3s_2s_1s_0$	1 1 0 0 1	$(25)_{10}$

Full adder circuit

C_i	X_i	Y_i	C_{i+1}	S_{i+1}
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$C_i \backslash X_i Y_i$	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S_i = X_i \oplus Y_i \oplus C_i$$


$C_i \backslash X_i Y_i$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_i = X_i Y_i + Y_i C_i + X_i C_i$$


Full adder circuit

 

Full adder circuit (decomposed)

 

Block diagram

 


Detailed diagram

Ripple-carry adder

- In performing addition, we start from the least significant digit and add pairs of digits progressing to the most significant digit
- If a carry is produced in position i , it is added to operands (digits) in position $i+1$
- A chain of full adders, connected in sequence, can perform this operation
- Such a configuration is called a ***ripple-carry adder*** because of the way the carry signal 'ripple' through from stage to stage

Ripple-carry adder

 




Ripple-carry adder

- Each full adder introduces a certain delay before its s_i and c_{i+1} outputs are valid
 - The propagation delay through the full adder
- Let this delay be Δt
- The carry out of the first stage c_1 arrives at the second stage Δt after the application of the x_0 and y_0 inputs
- The carry out of the second stage c_2 arrives at the third stage with a delay of $2\Delta t$, and so on
- The signal c_{n-1} is valid after $(n-1)\Delta t$, and the complete sum is available after a delay of $(n)\Delta t$
- The delay obviously depends on the size of the numbers (*i.e.* the number of bits)

Signed numbers

 - For signed numbers, in the binary system, the sign of the number is denoted by the left-most bit
 - 0 = positive
 - 1 = negative
- For an n -bit number, the remaining $n-1$ bits represent the magnitude



Negative numbers

- For signed numbers, there are three common formats for representing negative numbers
 - Sign-magnitude
 - 1's complement
 - 2's complement
- Sign-magnitude uses one bit for the sign (0=+, 1=-) and the remaining bits represent the magnitude of the number as in the case of unsigned numbers
- For example, using 4-bit numbers
 - +5=0101 -5=1101
 - +3=0011 -3=1011
 - +7=0111 -7=1111
- Although this is easy to understand, it is not well suited for use in computers

1's complement representation

- In the 1's complement scheme, an n -bit negative number K , is obtained by subtracting its equivalent positive number, P , from 2^n-1
$$K=(2^n-1)-P$$
- For example, if $n=4$, then
$$K=(2^4-1)-P=(15)_{10}-P=(1111)_2-P$$
$$-5=(15)_{10}-5=(1111)_2-(0101)_2=(1010)_2$$
$$-3=(15)_{10}-3=(1111)_2-(0011)_2=(1100)_2$$
- From these examples, clearly the 1's complement can be formed simply by complementing each bit of the number, including the sign bit
- Numbers in the 1's complement form have some drawbacks when used in arithmetic operations

2's complement representation

- In the 2's complement scheme, an n -bit negative number K , is obtained by subtracting its equivalent positive number, P , from 2^n
$$K = 2^n - P$$
- For example, if $n=4$, then
$$K = 2^4 - P = (16)_{10} - P = (10000)_2 - P$$
$$-5 = (16)_{10} - 5 = (10000)_2 - (0101)_2 = (1011)_2$$
$$-3 = (16)_{10} - 3 = (10000)_2 - (0011)_2 = (1101)_2$$
- A simple way of finding the 2's complement of a number is to add 1 to its 1's complement

Rule for finding 2's complements

- Given a signed number, $B = b_{n-1}b_{n-2} \dots b_1b_0$, its 2's complement, $K = k_{n-1}k_{n-2} \dots k_1k_0$, can be found by:
 - examining all the bits of B from right to left and complementing all the bits after the first '1' is encountered
- For example if
 $B = 00110100$
- Then the 2's complement of B is
 $K = 11001100$

changed bits unchanged bits



Four-bit signed integers

$b_3b_2b_1b_0$	Sign-magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Addition and subtraction

- For sign-magnitude numbers, addition is simple, but if the numbers have different signs the task becomes more complicated
 - Logic circuits that compare and subtract numbers are also needed
 - It is possible to perform subtraction without this circuitry
 - For this reason, sign-magnitude is not used in computers
- For 1's complement numbers, adding or subtracting some numbers may require a correction to obtain the actual binary result
- For example, $(-5) + (-2) = (-7)$, but when adding the binary equivalents of -5 and -2 , the result is 0111 with an additional carry out of 1 which must be added back to the result to produce the final (correct) result of 1000

2's complement operations

- For addition, the result is always correct
- Any carry-out from the sign-bit position is simply ignored

$$\begin{array}{r} (+5) \quad 0101 \\ + (+2) \quad 0010 \\ \hline (+7) \quad 0111 \end{array}$$

$$\begin{array}{r} (-5) \quad 1011 \\ + (+2) \quad 0010 \\ \hline (-3) \quad 1101 \end{array}$$

$$\begin{array}{r} (+5) \quad 0101 \\ + (-2) \quad 1110 \\ \hline (+3) \quad 10011 \end{array}$$

↑
ignore

$$\begin{array}{r} (-5) \quad 1011 \\ + (-2) \quad 1110 \\ \hline (-7) \quad 11001 \end{array}$$

↑
ignore

2's complement subtraction

- The easiest way of performing subtraction is to negate the subtrahend and add it to the minuend
 - Find the 2's complement of the subtrahend and then perform addition


$$\begin{array}{r} (+5) \\ - (+2) \\ \hline (+3) \end{array} \quad \begin{array}{r} 0101 \\ - 0010 \\ \hline \end{array} \Rightarrow \begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \\ \uparrow \\ \text{ignore} \end{array}$$

$$\begin{array}{r} (-5) \\ - (-2) \\ \hline (-3) \end{array} \quad \begin{array}{r} 1011 \\ - 1110 \\ \hline \end{array} \Rightarrow \begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array}$$

Adder and subtractor unit

- The subtraction operation can be realized as the addition operation, using a 2's complement of the subtrahend, regardless of the signs of the two operands
 - It is possible to use the same adder circuit to perform both addition and subtraction
- Recall that the 2's complement can be formed from the 1's complement simply by adding 1
- We can use the XOR operation to perform a 1's complement
 - Recall $x \oplus 1 = x'$ and $x \oplus 0 = x$
 - If we are performing a subtract operation, 1's complement the subtrahend by XORing each bit with 1

Adder and subtractor unit

 

Arithmetic overflow

- The result of addition or subtraction is supposed to fit within the significant bits used to represent the numbers
- If n bits are used to represent signed numbers, then the result must be in the range -2^{n-1} to $+2^{n-1}-1$
- If the result does not fit in this range, we say that ***arithmetic overflow*** has occurred
- To insure correct operation of an arithmetic circuit, it is important to be able to detect the occurrence of overflow

Examples for determining arithmetic overflow

For 4-bit numbers, there are 3 significant bits and the sign bit

$$\begin{array}{r} (+7) \quad \quad 0 \ 1 \ 1 \ 1 \\ + (+2) \quad + 0 \ 0 \ 1 \ 0 \\ \hline (+9) \quad \quad 1 \ 0 \ 0 \ 1 \\ c_4 = 0 \\ c_3 = 1 \end{array}$$

$$\begin{array}{r} (-7) \quad \quad 1 \ 0 \ 0 \ 1 \\ + (+2) \quad + 0 \ 0 \ 1 \ 0 \\ \hline (-5) \quad \quad 1 \ 0 \ 1 \ 1 \\ c_4 = 0 \\ c_3 = 0 \end{array}$$

$$\begin{array}{r} (+7) \quad \quad 0 \ 1 \ 1 \ 1 \\ + (-2) \quad + 1 \ 1 \ 1 \ 0 \\ \hline (+5) \quad \quad 1 \ 0 \ 1 \ 0 \ 1 \\ c_4 = 1 \\ c_3 = 1 \end{array}$$

$$\begin{array}{r} (-7) \quad \quad 1 \ 0 \ 0 \ 1 \\ + (-2) \quad + 1 \ 1 \ 1 \ 0 \\ \hline (-9) \quad \quad 1 \ 0 \ 1 \ 1 \ 1 \\ c_4 = 1 \\ c_3 = 0 \end{array}$$

If the numbers have different signs, no overflow can occur

Arithmetic overflow

- In the previous examples, overflow was detected by

$$\text{overflow} = c_3c_4' + c_3'c_4$$

$$\text{overflow} = c_3 \oplus c_4$$

- For n-bit numbers we have

$$\text{overflow} = c_{n-1} \oplus c_n$$

- The adder/subtractor circuit introduced can be modified to include overflow checking with the addition of one XOR gate