

# Registers and Counters

Chapter 06


Digital Design 4<sup>th</sup> Ed. by

Morris Mano

# Registers

- Registers and Counters are types of Sequential Circuits.
- A REGISTER is a group of flip-flops
- An n-bit register consists of n flip-flops, capable of storing n-bits of binary information
- In addition to flip-flops, registers may have additional combinational circuits for performing certain data processing tasks.

# Registers

 

**Fig 6-1**  
4-bit register

# Register with Parallel Load

Load

 


Fig 5-2  
4-bit Register with Parallel Load

# Register with Parallel Load

Load = 0

$$D_0 = A_0$$

No new data will be stored. Old data ( $A_0$ ) will be refreshed and retained.

 


Fig 5-1  
4-bit Register with Parallel Load

# Register with Parallel Load

Load = 1

$$D_0 = I_0$$

New data  $I_0$  will be stored on next clock edge.


 


Fig 5-1  
4-bit Register with Parallel Load

# Shift Register

- A register capable of shifting its binary information in one or both directions.
- Can be used for serial transfers


# Shift Register

 


**Fig 6-3**




# Shift Register

 


**Fig 6-3**

 

# Shift Register

 

**Fig 6-3**

 

**COUNTERS**

# Counters

- A counter is essentially a register that goes through a predetermined sequence states on the application of input.
  - The input can be a clock pulse or any other input.
- The gates in the counter are connected in such a way as to produce the prescribed sequence of binary states.

# Counters - Categories

## 1. Ripple Counter

- The flip flop output transitions serve as a source of triggering other flip-flops
- i.e. C input of some or all flip-flops is not triggered by the common clock pulse

## 2. Synchronous Counter

- C input of all flip flops is connected to same clock input



# Binary Ripple Counter

- A counter that follows the binary number sequence is called a BINARY COUNTER.
- A BINARY RIPPLE COUNTER consists of a series connection of complementing flip-flops, with the output of each flip-flop connected to the C input of the next flip-flop.
- The flip-flop holding the least significant bit is given an input clock pulse.
  
# Ripple Counter


- **How does it work?**

- When there is a positive edge on the clock input of A, A complements
- The clock input for flip-flop B is the complemented output of flip-flop A
- When flip A changes from 1 to 0, there is a positive edge on the clock input of B causing B to complement


 
# Ripple Counter (continued)

- The arrows show the cause-effect relationship from the prior slide
- The corresponding sequence of states  $(B,A) = (0,0), (0,1), (1,0), (1,1), (0,0), (0,1), \dots$
- Each additional bit, C, D, ... behaves like bit B, changing half as frequently as the bit before it.
- For 3 bits:  $(C,B,A) = (0,0,0), (0,0,1), (0,1,0), (0,1,1), (1,0,0), (1,0,1), (1,1,0), (1,1,1), (0,0,0), \dots$






# Ripple Counter (continued)


- These circuits are called *ripple counters* because each edge sensitive transition (positive in the example) causes a change in the next flip-flop's state.
- The changes “ripple” upward through the chain of flip-flops, i. e., each transition occurs after a clock-to-output delay from the stage before.
- To see this effect in detail look at the waveforms on the next slide.

# Binary Ripple Counter with J-K Flip Flops


| A3 | A2 | A1 | A0 |
|----|----|----|----|
| 0  | 0  | 0  | 0  |
| 0  | 0  | 0  | 1  |
| 0  | 0  | 1  | 0  |
| 0  | 0  | 1  | 1  |
| 0  | 1  | 0  | 0  |
| 0  | 1  | 0  | 1  |
| 0  | 1  | 1  | 0  |
| 0  | 1  | 1  | 1  |
| 1  | 0  | 0  | 0  |
| 1  | 0  | 0  | 1  |
| 1  | 0  | 1  | 0  |
| 1  | 0  | 1  | 1  |
| 1  | 1  | 0  | 0  |
| 1  | 1  | 0  | 1  |
| 1  | 1  | 1  | 0  |
| 1  | 1  | 1  | 1  |
| 0  | 0  | 0  | 0  |

 

# Binary Ripple Counter

 

# BCD-Ripple Counter

 

# BCD-Ripple Counter

| <u>Present State</u> |   |   |   |  | <u>Next State</u> |   |   |   |
|----------------------|---|---|---|--|-------------------|---|---|---|
| A                    | B | C | D |  | A                 | B | C | D |
| 0                    | 0 | 0 | 0 |  | 0                 | 0 | 0 | 1 |
| 0                    | 0 | 0 | 1 |  | 0                 | 0 | 1 | 0 |
| 0                    | 0 | 1 | 0 |  | 0                 | 0 | 1 | 1 |
| 0                    | 0 | 1 | 1 |  | 0                 | 1 | 0 | 0 |
| 0                    | 1 | 0 | 0 |  | 0                 | 1 | 0 | 1 |
| 0                    | 1 | 0 | 1 |  | 0                 | 1 | 1 | 0 |
| 0                    | 1 | 1 | 0 |  | 0                 | 1 | 1 | 1 |
| 0                    | 1 | 1 | 1 |  | 1                 | 0 | 0 | 0 |
| 1                    | 0 | 0 | 0 |  | 1                 | 0 | 0 | 1 |
| 1                    | 0 | 0 | 1 |  | 0                 | 0 | 0 | 0 |

# BCD-Ripple Counter

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |

Present State

Next State

# BCD-Ripple Counter

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |

Present State

Next State

# BCD-Ripple Counter

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |

Present State

Next State

# BCD-Ripple Counter

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |

Present State

Next State

# BCD-Ripple Counter


| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 |

Present State

Next State


# BCD-Ripple Counter

| D |
|---|
| 0 |
| 1 |
| 0 |
| 1 |
| 0 |
| 1 |
| 0 |
| 1 |
| 0 |
| 1 |
| 0 |

 

# BCD-Ripple Counter

| C | D |
|---|---|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| 1 | 1 |
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| 1 | 1 |
| 0 | 0 |
| 0 | 1 |
| 0 | 0 |

 

# BCD-Ripple Counter

| BCD |    |    |    |
|-----|----|----|----|
| Q8  | Q4 | Q2 | Q1 |
| 0   | 0  | 0  | 0  |
| 0   | 0  | 0  | 1  |
| 0   | 0  | 1  | 0  |
| 0   | 0  | 1  | 1  |
| 0   | 1  | 0  | 0  |
| 0   | 1  | 0  | 1  |
| 0   | 1  | 1  | 0  |
| 0   | 1  | 1  | 1  |
| 1   | 0  | 0  | 0  |
| 1   | 0  | 0  | 1  |
| 0   | 0  | 0  | 0  |

 


Fig 6-14  
BCD ripple counter


# BCD-Ripple Counter

| BCD |    |    |    |
|-----|----|----|----|
| Q8  | Q4 | Q2 | Q1 |
| 0   | 0  | 0  | 0  |
| 0   | 0  | 0  | 1  |
| 0   | 0  | 1  | 0  |
| 0   | 0  | 1  | 1  |
| 0   | 1  | 0  | 0  |
| 0   | 1  | 0  | 1  |
| 0   | 1  | 1  | 0  |
| 0   | 1  | 1  | 1  |
| 1   | 0  | 0  | 0  |
| 1   | 0  | 0  | 1  |
| 0   | 0  | 0  | 0  |

- Q1 triggers FF<sub>2</sub> and FF<sub>8</sub>
- K of all are logic 1
- J<sub>1</sub> is logic 1
- J<sub>2</sub> is Q<sub>8</sub>'
- J<sub>4</sub> is logic 1
- J<sub>8</sub> is Q<sub>2</sub>Q<sub>4</sub>

# BCD-Ripple Counter

| BCD |    |    |    |
|-----|----|----|----|
| Q8  | Q4 | Q2 | Q1 |
| 0   | 0  | 0  | 0  |
| 0   | 0  | 0  | 1  |
| 0   | 0  | 1  | 0  |
| 0   | 0  | 1  | 1  |
| 0   | 1  | 0  | 0  |
| 0   | 1  | 0  | 1  |
| 0   | 1  | 1  | 0  |
| 0   | 1  | 1  | 1  |
| 1   | 0  | 0  | 0  |
| 1   | 0  | 0  | 1  |
| 0   | 0  | 0  | 0  |

 

**Fig 6-14**  
BCD ripple counter



# BCD-Ripple Counter

- $Q_1$  triggers  $FF_2$  and  $FF_8$
- K of all are logic 1
- $J_1$  is logic 1
- $J_2$  is  $Q_8'$
- $J_4$  is logic 1
- $J_8$  is  $Q_2 Q_4$


 


Fig 6-14  
BCD ripple counter

# 4-bit Binary Synchronous Counter

 


# 4-bit Binary Synchronous Counter

| Present State |    |    |    |  | Next State |    |    |    |
|---------------|----|----|----|--|------------|----|----|----|
| A3            | A2 | A1 | A0 |  | A3         | A2 | A1 | A0 |
| 0             | 0  | 0  | 0  |  | 0          | 0  | 0  | 1  |
| 0             | 0  | 0  | 1  |  | 0          | 0  | 1  | 0  |
| 0             | 0  | 1  | 0  |  | 0          | 0  | 1  | 1  |
| 0             | 0  | 1  | 1  |  | 0          | 1  | 0  | 0  |
| 0             | 1  | 0  | 0  |  | 0          | 1  | 0  | 1  |
| 0             | 1  | 0  | 1  |  | 0          | 1  | 1  | 0  |
| 0             | 1  | 1  | 0  |  | 0          | 1  | 1  | 1  |
| 0             | 1  | 1  | 1  |  | 1          | 0  | 0  | 0  |
| 1             | 0  | 0  | 0  |  | 1          | 0  | 0  | 1  |
| 1             | 0  | 0  | 1  |  | 1          | 0  | 1  | 0  |
| 1             | 0  | 1  | 0  |  | 1          | 0  | 1  | 1  |
| 1             | 0  | 1  | 1  |  | 1          | 1  | 0  | 0  |
| 1             | 1  | 0  | 0  |  | 1          | 1  | 0  | 1  |
| 1             | 1  | 0  | 1  |  | 1          | 1  | 1  | 0  |
| 1             | 1  | 1  | 0  |  | 1          | 1  | 1  | 1  |
| 1             | 1  | 1  | 1  |  | 0          | 0  | 0  | 0  |

# 4-bit Binary Synchronous Counter

| Present State |    |    |    |  | Next State |    |    |    |  | Inputs to Flip Flops |    |    |    |    |    |    |    |
|---------------|----|----|----|--|------------|----|----|----|--|----------------------|----|----|----|----|----|----|----|
| A3            | A2 | A1 | A0 |  | A3         | A2 | A1 | A0 |  | J3                   | K3 | J2 | K2 | J1 | K1 | J0 | K0 |
| 0             | 0  | 0  | 0  |  | 0          | 0  | 0  | 1  |  | 0                    | X  | 0  | X  | 0  | X  | 1  | X  |
| 0             | 0  | 0  | 1  |  | 0          | 0  | 1  | 0  |  | 0                    | X  | 0  | X  | 1  | X  | X  | 1  |
| 0             | 0  | 1  | 0  |  | 0          | 0  | 1  | 1  |  | 0                    | X  | 0  | X  | X  | 0  | 1  | X  |
| 0             | 0  | 1  | 1  |  | 0          | 1  | 0  | 0  |  | 0                    | X  | 1  | X  | X  | 1  | X  | 1  |
| 0             | 1  | 0  | 0  |  | 0          | 1  | 0  | 1  |  | 0                    | X  | X  | 0  | 0  | X  | 1  | X  |
| 0             | 1  | 0  | 1  |  | 0          | 1  | 1  | 0  |  | 0                    | X  | X  | 0  | 1  | X  | X  | 1  |
| 0             | 1  | 1  | 0  |  | 0          | 1  | 1  | 1  |  | 0                    | X  | X  | 0  | X  | 0  | 1  | X  |
| 0             | 1  | 1  | 1  |  | 1          | 0  | 0  | 0  |  | 1                    | X  | X  | 1  | X  | 1  | X  | 1  |
| 1             | 0  | 0  | 0  |  | 1          | 0  | 0  | 1  |  | X                    | 0  | 0  | X  | 0  | X  | 1  | X  |
| 1             | 0  | 0  | 1  |  | 1          | 0  | 1  | 0  |  | X                    | 0  | 0  | X  | 1  | X  | X  | 1  |
| 1             | 0  | 1  | 0  |  | 1          | 0  | 1  | 1  |  | X                    | 0  | 0  | X  | X  | 0  | 1  | X  |
| 1             | 0  | 1  | 1  |  | 1          | 1  | 0  | 0  |  | X                    | 0  | 1  | X  | X  | 1  | X  | 1  |
| 1             | 1  | 0  | 0  |  | 1          | 1  | 0  | 1  |  | X                    | 0  | X  | 0  | 0  | X  | 1  | X  |
| 1             | 1  | 0  | 1  |  | 1          | 1  | 1  | 0  |  | X                    | 0  | X  | 0  | 1  | X  | X  | 1  |
| 1             | 1  | 1  | 0  |  | 1          | 1  | 1  | 1  |  | X                    | 0  | X  | 0  | X  | 0  | 1  | X  |
| 1             | 1  | 1  | 1  |  | 0          | 0  | 0  | 0  |  | X                    | 1  | X  | 1  | X  | 1  | X  | 1  |

# 4-bit Binary Synchronous Counter

 


| A3 | A2 | A1 | A0 |
|----|----|----|----|
| 0  | 0  | 0  | 0  |
| 0  | 0  | 0  | 1  |
| 0  | 0  | 1  | 0  |
| 0  | 0  | 1  | 1  |
| 0  | 1  | 0  | 0  |
| 0  | 1  | 0  | 1  |
| 0  | 1  | 1  | 0  |
| 0  | 1  | 1  | 1  |
| 1  | 0  | 0  | 0  |
| 1  | 0  | 0  | 1  |
| 1  | 0  | 1  | 0  |
| 1  | 0  | 1  | 1  |
| 1  | 1  | 0  | 0  |
| 1  | 1  | 0  | 1  |
| 1  | 1  | 1  | 0  |
| 1  | 1  | 1  | 1  |
| 0  | 0  | 0  | 0  |

Fig  
4-bi
 
# Synchronous Counters (continued)

- Internal Logic
  - XOR complements each bit
  - AND chain causes complement of a bit if all bits toward LSB from it equal 1
- Count Enable
  - Forces all outputs of AND chain to 0 to “hold” the state
- Carry Out
  - Added as part of incrementer
  - Connect to Count Enable of additional 4-bit counters to form larger counters




Cloc

t CO

# Synchronous Counters (continued)

| A3 | A2 | A1 | A0 |
|----|----|----|----|
| 0  | 0  | 0  | 0  |
| 0  | 0  | 0  | 1  |
| 0  | 0  | 1  | 0  |
| 0  | 0  | 1  | 1  |
| 0  | 1  | 0  | 0  |
| 0  | 1  | 0  | 1  |
| 0  | 1  | 1  | 0  |
| 0  | 1  | 1  | 1  |
| 1  | 0  | 0  | 0  |
| 1  | 0  | 0  | 1  |
| 1  | 0  | 1  | 0  |
| 1  | 0  | 1  | 1  |
| 1  | 1  | 0  | 0  |
| 1  | 1  | 0  | 1  |
| 1  | 1  | 1  | 0  |
| 1  | 1  | 1  | 1  |
| 0  | 0  | 0  | 0  |

 


Cloc

t CO

# Counter with Parallel Load

- Add path for input data
  - enabled for Load = 1
- Add logic to:
  - disable count logic for Load = 1
  - disable feedback from outputs for Load = 1
  - enable count logic for Load = 0 and Count = 1
- The resulting function table:

| Load | Count | Action                |
|------|-------|-----------------------|
| 0    | 0     | Hold Stored Value     |
| 0    | 1     | Count Up Stored Value |
| 1    | X     | Load D                |

 



# Design Example: Synchronous BCD

- Use the sequential logic model to design a synchronous BCD counter with D flip-flops
- State Table =>
- Input combinations 1010 through 1111 are don't cares

| Current State | Next State  |
|---------------|-------------|
| Q3 Q2 Q1 Q0   | Q3 Q2 Q1 Q0 |
| 0 0 0 0       | 1 0 0 1     |
| 0 0 0 1       | 0 0 0 1     |
| 0 0 1 0       | 1 0 1 0     |
| 0 0 1 1       | 0 0 1 1     |
| 0 1 0 0       | 1 1 0 0     |
| 0 1 0 1       | 0 1 0 0     |
| 0 1 1 0       | 1 0 0 0     |
| 0 1 1 1       | 0 0 0 0     |
| 1 0 0 0       | 0 0 0 0     |
| 1 0 0 1       | 0 0 0 0     |
| 1 0 1 0       | 0 0 0 0     |
| 1 0 1 1       | 0 0 0 0     |
| 1 1 0 0       | 0 0 0 0     |
| 1 1 0 1       | 0 0 0 0     |
| 1 1 1 0       | 0 0 0 0     |
| 1 1 1 1       | 0 0 0 0     |

# Synchronous BCD (continued)

- Use K-Maps to two-level optimize the next state equations and manipulate into forms containing XOR gates:

$$D1 = Q1$$

$$D2 = Q2 + Q1Q8$$

$$D4 = Q4 + Q1Q2$$


$$D8 = Q8 + (Q1Q8 + Q1Q2Q4)$$

- The logic diagram can be draw from these equations
  - An asynchronous or synchronous reset should be added
- What happens if the counter is perturbed by a power disturbance or other interference and it enters a state other than 0000 through 1001?

# Synchronous BCD (continued)

- Find the actual values of the six next states for the don't care combinations from the equations
- Find the overall state diagram to assess behavior for the don't care states (states in decimal)

| Present State |    |    |    | Next State |    |    |    |
|---------------|----|----|----|------------|----|----|----|
| Q8            | Q4 | Q2 | Q1 | Q8         | Q4 | Q2 | Q1 |
| 1             | 0  | 1  | 0  | 1          | 0  | 1  | 1  |
| 1             | 0  | 1  | 1  | 0          | 1  | 1  | 0  |
| 1             | 1  | 0  | 0  | 1          | 1  | 0  | 1  |
| 1             | 1  | 0  | 1  | 0          | 1  | 0  | 0  |
| 1             | 1  | 1  | 0  | 1          | 1  | 1  | 1  |
| 1             | 1  | 1  | 1  | 0          | 0  | 1  | 0  |

 


# Synchronous BCD (continued)

- For the BCD counter design, if an invalid state is entered, return to a valid state occurs within two clock cycles
- Is this adequate? If not:
  - Is a signal needed that indicates that an invalid state has been entered? What is the equation for such a signal?
  - Does the design need to be modified to return from an invalid state to a valid state in one clock cycle?
  - Does the design need to be modified to return from a invalid state to a specific state (such as 0)?
- The action to be taken depends on:
  - the application of the circuit
  - design group policy

# Ring Counter

| Clock | Q0 | Q1 | Q2 | Q3 |
|-------|----|----|----|----|
| 0     | 1  | 0  | 0  | 0  |
| 1     | 0  | 1  | 0  | 0  |
| 2     | 0  | 0  | 1  | 0  |
| 3     | 0  | 0  | 0  | 1  |
| 4     | 1  | 0  | 0  | 0  |

 

# Johnson Counter

| Clock | Q0 | Q1 | Q2 | Q3 |
|-------|----|----|----|----|
| 0     | 0  | 0  | 0  | 0  |
| 1     | 1  | 0  | 0  | 0  |
| 2     | 1  | 1  | 0  | 0  |
| 3     | 1  | 1  | 1  | 0  |
| 4     | 1  | 1  | 1  | 1  |
| 5     | 0  | 1  | 1  | 1  |
| 6     | 0  | 0  | 1  | 1  |

