

Micro-programmed State Machines


Lecture 10

Dr. Shoab A. Khan

Micro-programmable State machines


- A Micro-Programmable State machine substitutes combinational cloud of FSM with Programmable Memory (PM)
- The control signals for all the states are stored and read from PM instead of being generated by combination logic

 PM-BASED MICRO-PROGRAMMABLE STATE MACHINE



- Mealy machine: PM address bits are function of Input and current states, the PM data bits are outputs and next state



Example Design

 

- 2-bit input and 4-bit current state constitutes 6-bit address of PM
- 9-bit wide PM contents are 5-bit output bits for control and 4-bit next state


Micro-programmed State Machine Implementation

  - Number of 1s detected problem of Chapter 9
- Combinational cloud is replaced by PM



Moore Machine

 - Number of 1s detected problem of Chapter 9
- Moore machine two combinational clouds are replaced by two PMs




Design Example: 4 Entry FIFO as Micro-program State machine

 1. Design a first-in, first-out (FIFO) queue that consists of four registers R0, R1, R2, and R3
2. Write and Delete are the two operations on the queue
3. Write moves data from the **fifo_in** to R0 that is the tail of the queue
4. Delete deletes the first entry at the head of the queue
5. The head of the queue is available on the **fifo_out**
6. Writing into a full queue or deletion from an empty queue causes an **ERROR** condition
7. Assertion of **Write** and **Delete** at the same time also causes an **ERROR** condition

FIFO Design

- Design consists of datapath and controller
- Datapath
 - Four registers
 - Shift registers
 - One 4:1 MUX
- Controller
 - Input signals
 - Write
 - Delete
 - Output signals
 - out_sel
 - write_en
 - Error




Controller

- FSM based design



- Mealy machine

- Five states

 
- S0: Idle
 - S1: One entry
 - S2: Two entries
 - S3: Three entries
 - S4: Full




FIFO/LIFO

  

Counter-based FSM: Bit serial adder

 

 
Counter-based State Machine Implementation




Modifications to Counter-based Microcontrollers 1

- Mechanism for changing count sequence
- Begin another sequence under control of micro-program memory


Loadable Counter for *Goto* capability

 

A Generic Computing Architecture

 


Example: Complete Design

 

Conditional Execution

- 2-bit control allowing on selection of two conditional inputs and two signals true and false
- The conditions come from the status register in the data path
- Example:
 - zero and positive flags are used for providing conditional execution
 - if ($r1 > r2$) jump label3; // compute $r1-r2$ jump if result is positive
 - if ($r1 == r2$) jump label1; // compute $r1-r2$, jump if result is zero
 - jump label 2 // unconditional jump

Conditional Branching Capability

 


Conditional load

sel	load
00	FALSE (normal execution: never load branch address)
01	COND0 (load branch address if COND0 is TRUE)
10	COND1 (load branch address if COND1 is TRUE)
11	TRUE (unconditional jump: always load branch address)

Pipelined Register

- Often counters are replaced with an ALU based program counter register
- The critical path of the design is long as it goes from the counter to ROM to architecture to functional units generating COND0 and COND1 to conditional MUX.
- The critical path can be broken by inserting a pipeline register in the design


Micro PC Based Controller

 


Conditional Branching with Parity

- Conditional execution
 - 2-bit control allowing on selection of two conditional inputs and two signals true and false.
 - A parity bit for inverse selection of the condition
 - Example:
 - zero and positive flags are used for providing conditional execution
 - Inverse selection is provided by parity bit
 - if ($r1 > r2$) jump label3; // compute $r1-r2$ jump if result is positive
 - if ($r1 < r2$) jump label3; // compute $r1-r2$ jump if result is negative (positive flag 0 and polarity bit is set)
 - if ($r1 == r2$) jump label1; // compute $r1-r2$, jump if result is zero
 - if ($r1 != r2$) jump label1; // compute $r1-r2$, jump if result is not zero (zero flag is 0 and polarity bit is set)
 - jump label 2 // unconditional jump



Addition of Parity bit

 

Controller with data path

 

Instruction word design

  

micro PC-based ASM with Conditional Multiplexer

