

EE-102 Electric Circuit Analysis

Experiment # 7

Assignment 1 Practicle Implementation

Objective/s:


- To verify Kirchoff's voltage and current laws

Components

- Resistors
- DMM
- DC power supply

1. Tasks

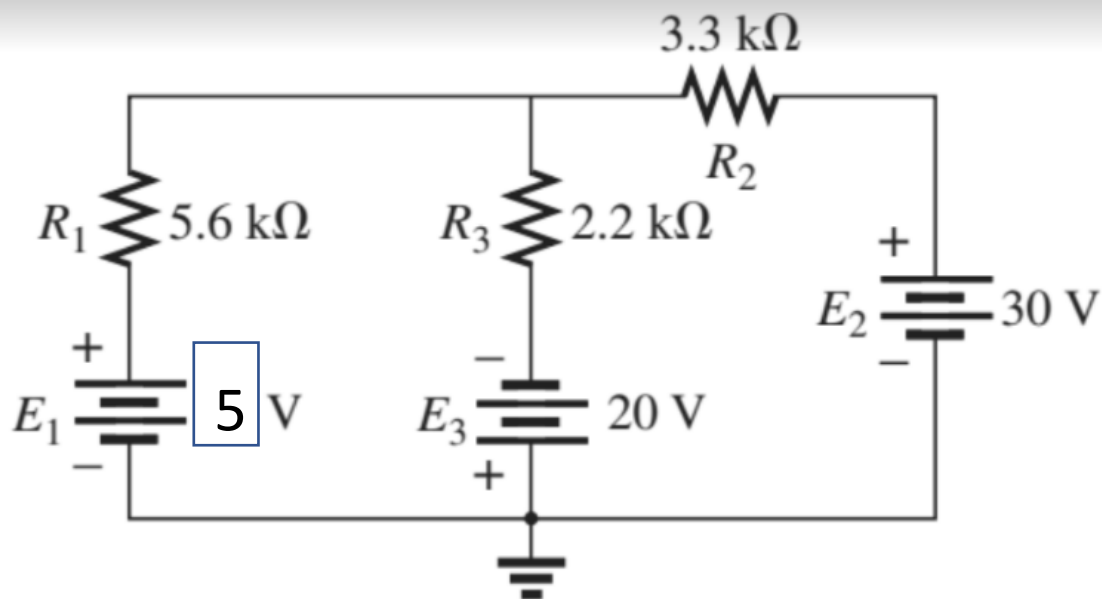1. Using branch-current analysis, find the current through each resistor for the network in Fig. 1. The resistors are all standard values.



2 Observations

	I_{Total}	I_{R1}	I_{R2}	I_{R3}	Sum
Calculated					
Measured					

Table 1