

EE-102 Electric Circuit Analysis

Experiment # 8

Assignment 1 Practical Implementation

Objective/s:


- To verify Kirchoff's voltage and current laws

Components

- Resistors
- DMM
- DC power supply

1. Tasks

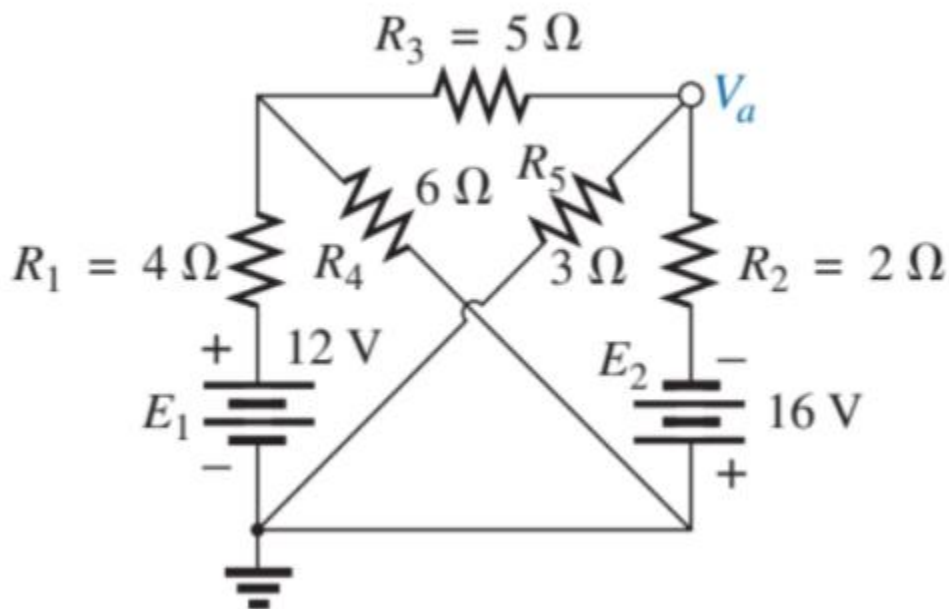1. Using mesh analysis, find the current through 50hm resistor and then determine voltage V_a in Fig. 1. The resistors are all standard values. Use the values of resistors as mentioned during lab experiment



2 Observations

	I_3	V_a
Calculated		
Measured		

Table 1