

EE-102 Electric Circuit Analysis

Experiment # 9


Bridge Circuits Analysis

Objective/s:

- To verify different bridge circuit configurations


Components

- Resistors
- DMM
- DC power supply

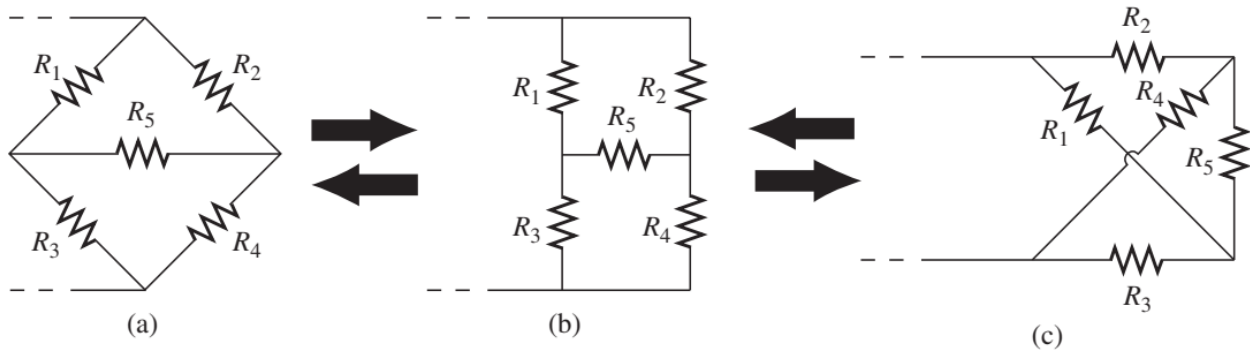

1. Tasks

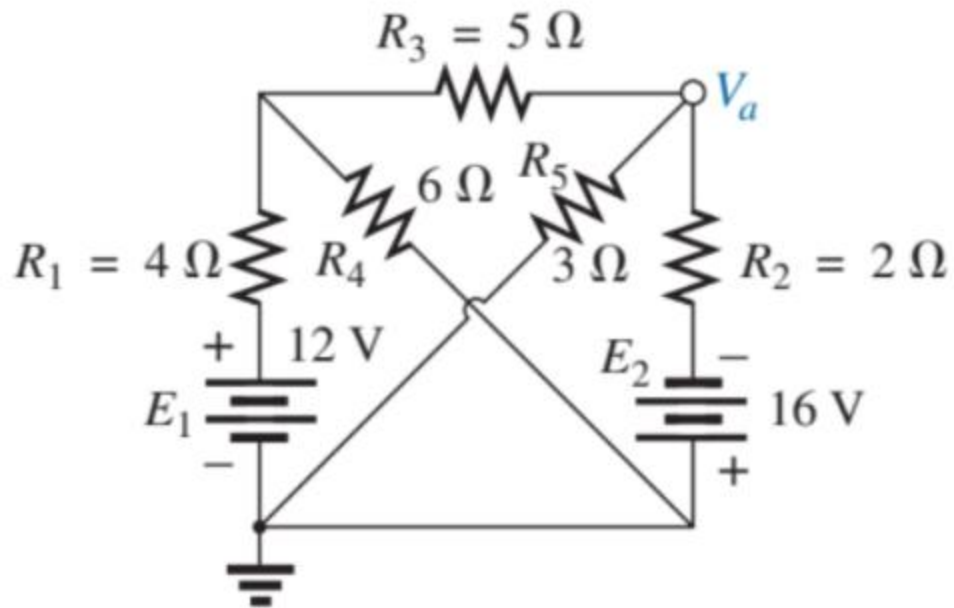1. Using Nodal Analysis prove that circuit in Fig b and c are the same by finding the current across R_5 (I_5). Plot a table and mention the calculated and measured mentioned current



2 Observations

	I_3	V_a
Calculated		
Measured		

Table 1